
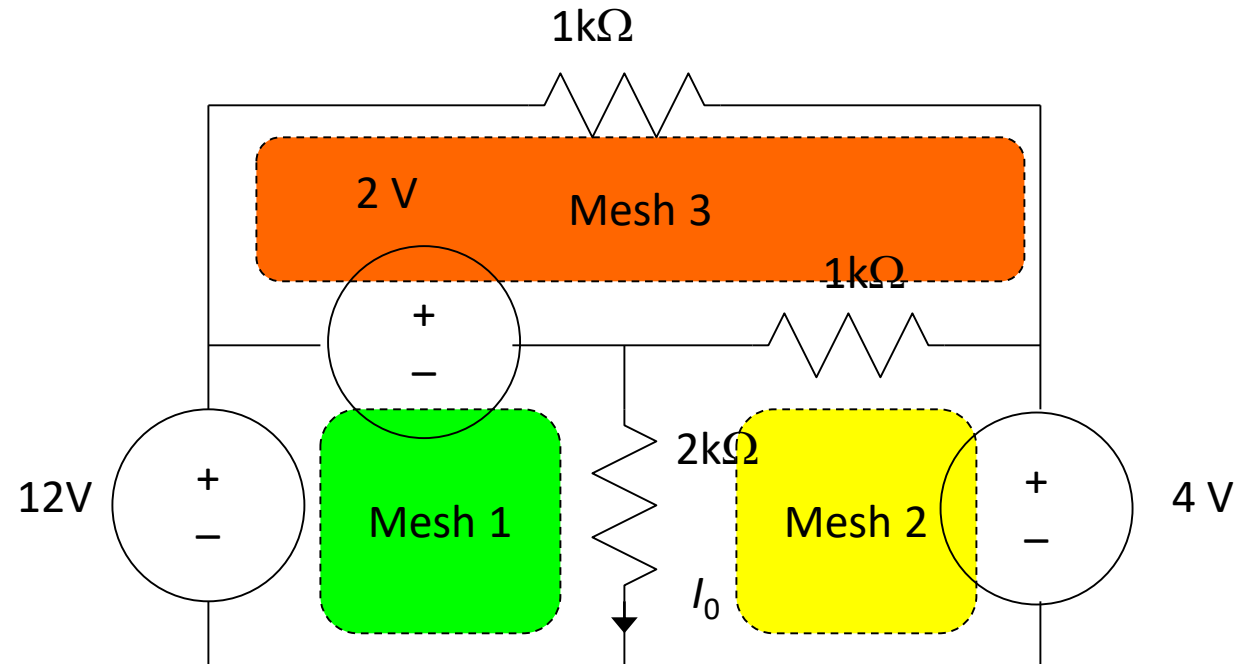


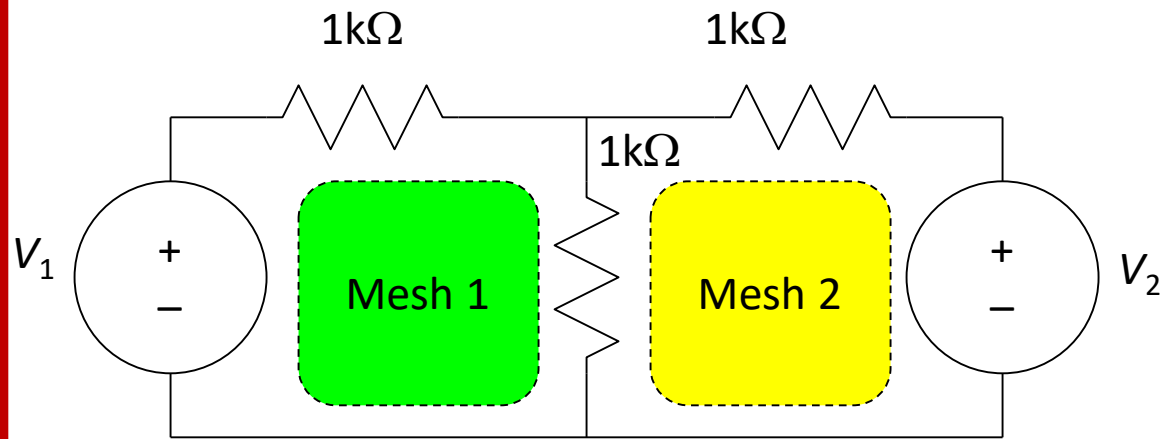

SATHYABAMA

Identifying the Meshes





By ohms law $V=IR$


If the circuit contains 2 loops
then matrix will be 2X2 matrix

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Where

R_{11}  Sum of the resistances in loop 1

R_{22}  Sum of the resistances in loop 2

R_{33}  Sum of the resistances in loop 3


$R_{31} = R_{13}$  Sum of the resistances in loop 1 and 3


$R_{12} = R_{21}$  Sum of the resistances in loop 1 and 2


$R_{32} = R_{23}$  Sum of the resistances in loop 2 and 3

If the circuit contains 3 loops
then matrix will be 3X3 matrix

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$


V_1  Sum of the voltages in loop 1

V_2  Sum of the voltages in loop 2

V_3  Sum of the voltages in loop 3

I_1  Unknown loop current in loop 1




I_2  Unknown loop current in loop 2

I_3  Unknown loop current in loop 3

Rules:


All the diagonal elements are positive (R_{11}, R_{22}, R_{33})

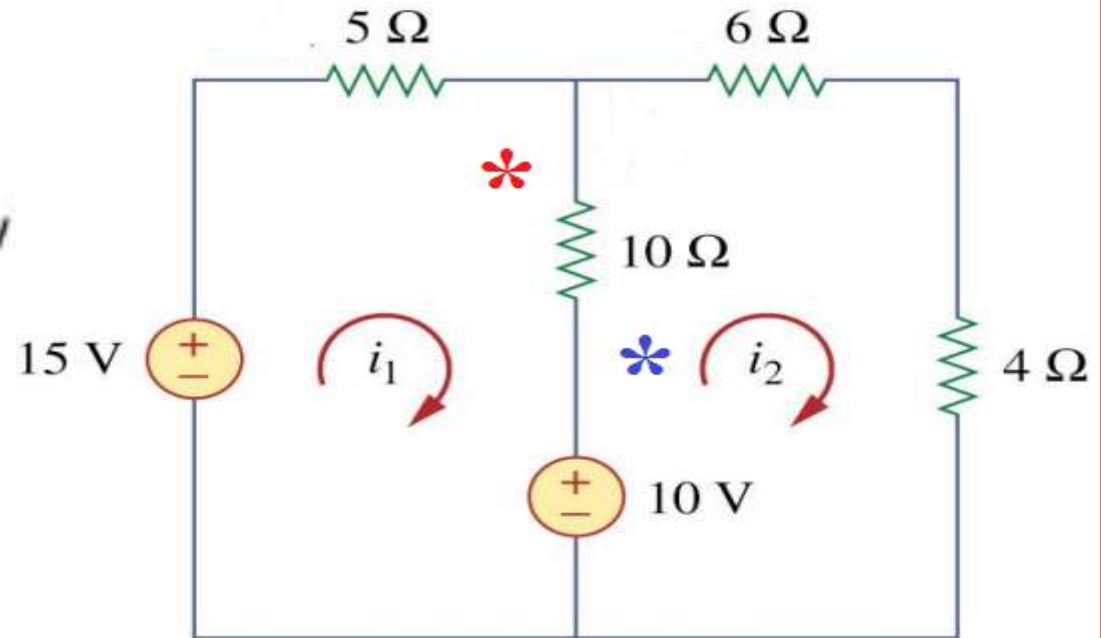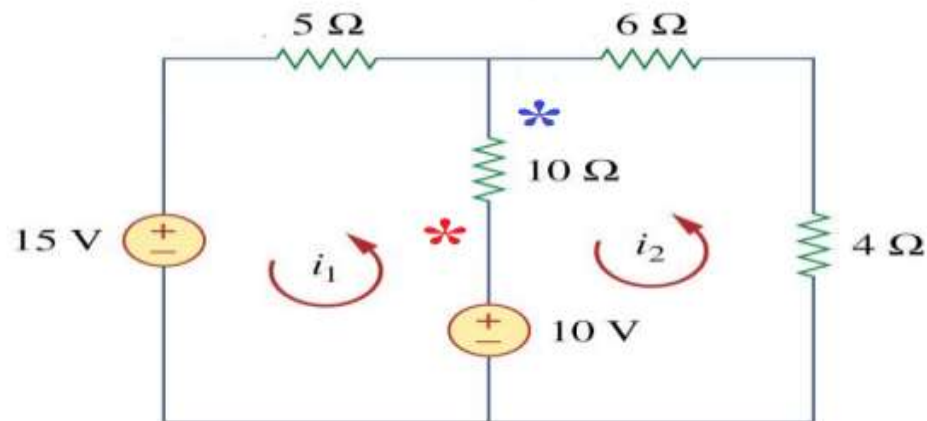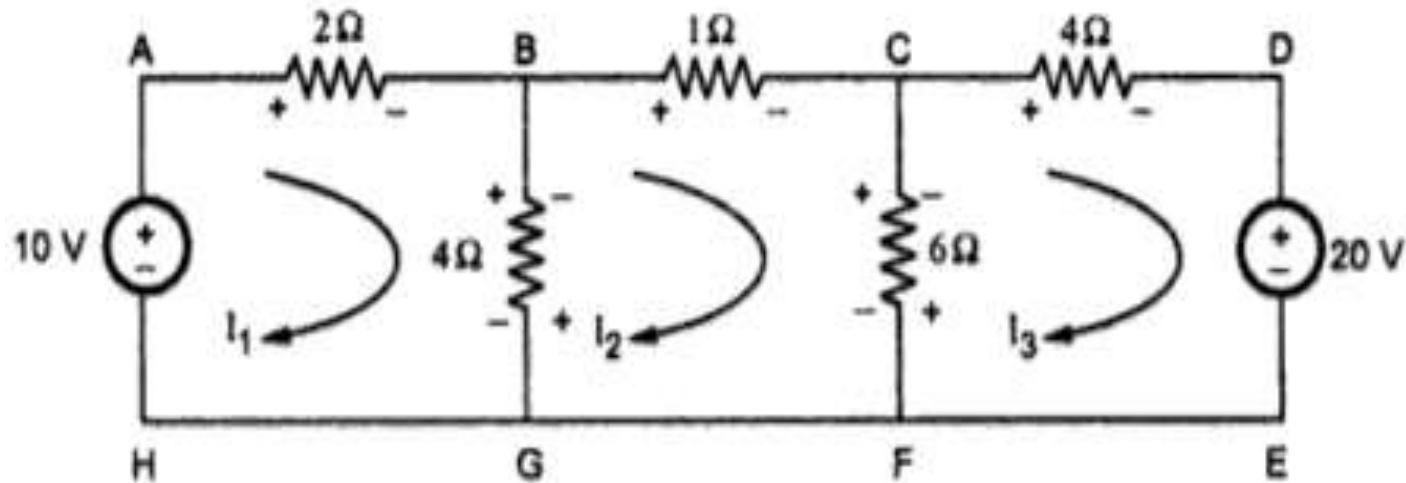All the Non diagonal elements ($R_{12}, R_{23}, R_{13}, R_{21}, R_{32}, R_{31}$) are Negative if all the loop currents are in the same direction




Rules continued

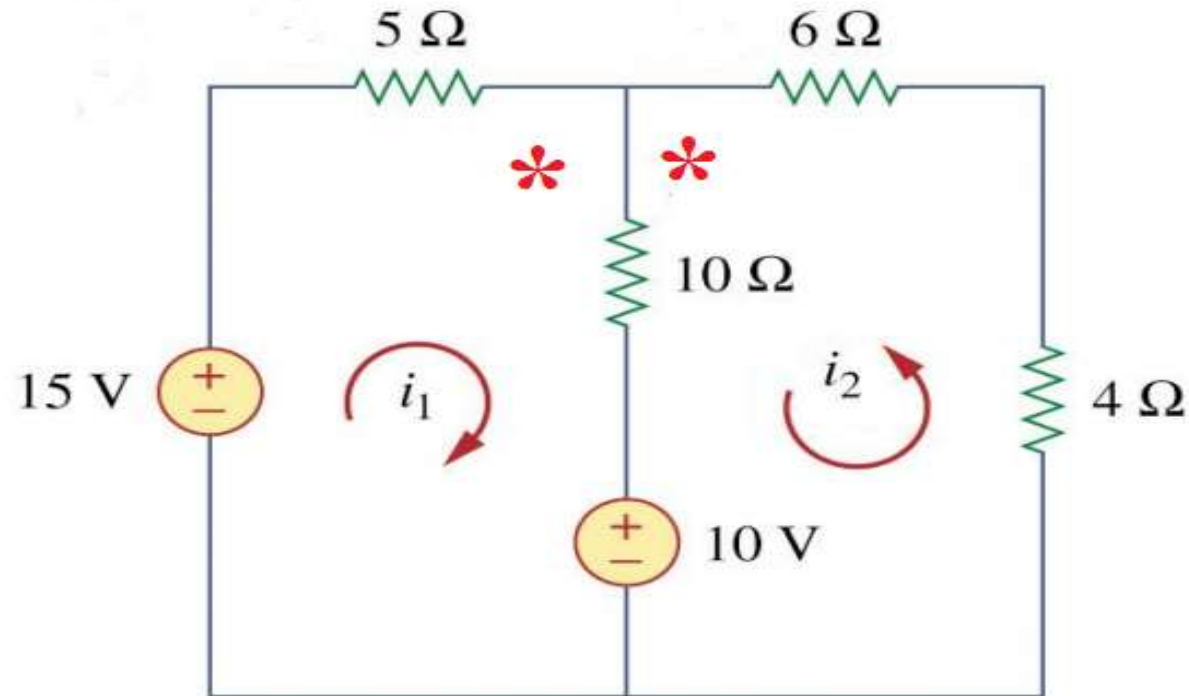The Non diagonal elements($R_{12}, R_{23}, R_{13}, R_{21}, R_{32}, R_{31}$) are positive if the loop currents in the common element aid each other.



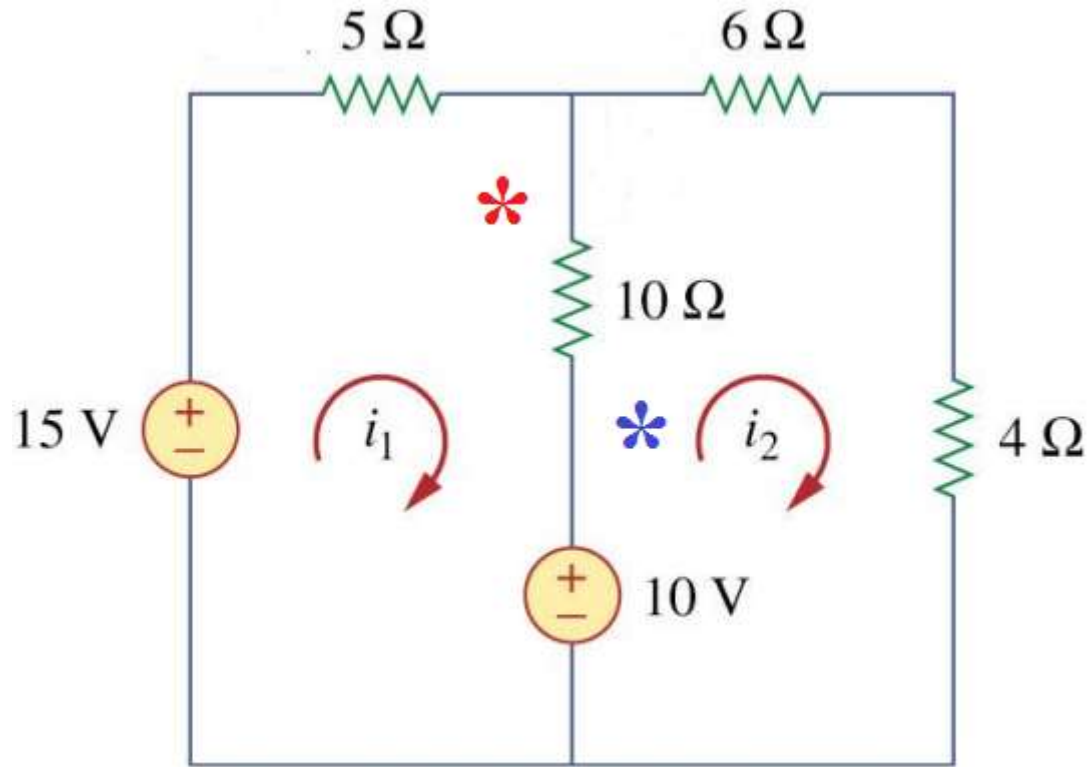Problem No.1

Solve the given circuit and find the mesh currents and branch currents and branch voltages.



Solution for Problem No.1


$$R_{11} = 5 + 10 = 15$$

$$R_{22} = 10 + 6 + 4 = 20$$

$$R_{12} = R_{21} = -10$$

$$V_1 = 15 - 10 = 5$$

$$V_2 = 10$$

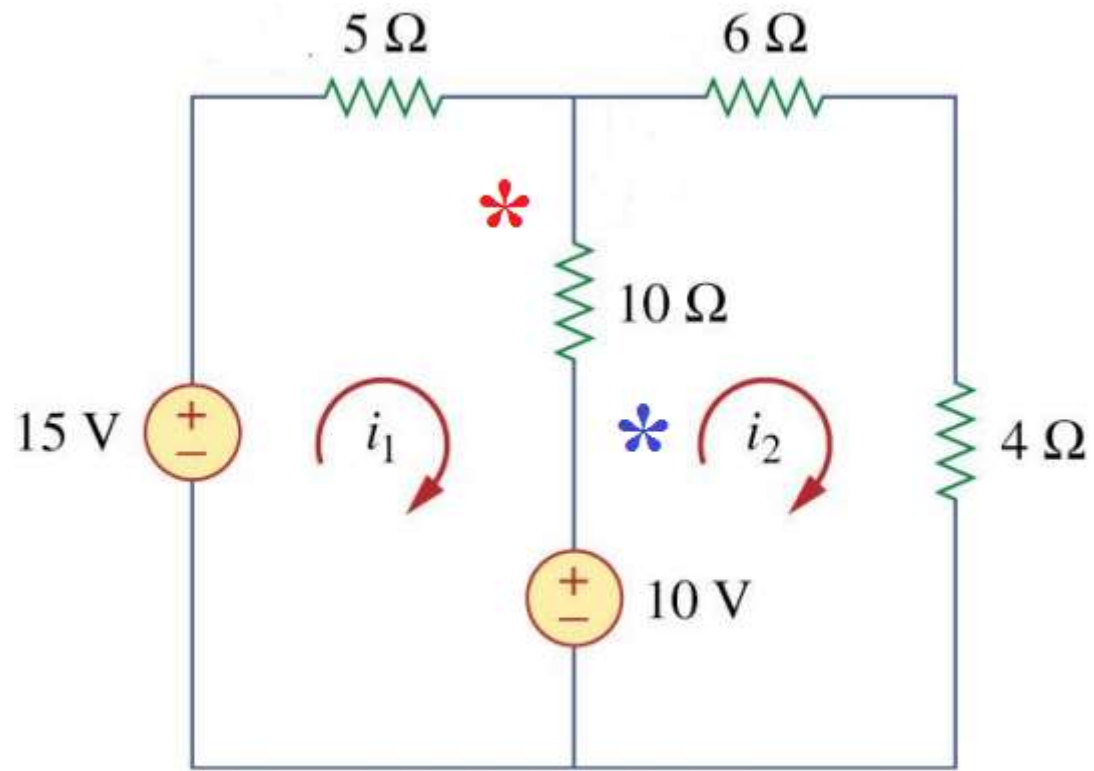

$$\begin{bmatrix} 15 & -10 \\ -10 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 15 & -10 \\ -10 & 20 \end{bmatrix} = 200$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{200}{200} = 1 \text{ Amps}$$

$$\Delta_1 = \begin{bmatrix} 5 & -10 \\ 10 & 20 \end{bmatrix} = 200$$

$$\Delta_2 = \begin{bmatrix} 15 & 5 \\ -10 & 10 \end{bmatrix} = 200$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{200}{200} = 1 \text{ Amps}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{200}{200} = 1 \text{ Amps}$$

Current in 5Ω Resistor = $I_1 = 1$ Amps

Current in 6Ω Resistor = $I_2 = 1$ Amps

Current in 4Ω Resistor = $I_2 = 1$ Amps


Current in 10Ω Resistor = $I_1 - I_2 = 0$ Amps


Voltage in 5Ω Resistor = $1 * 5 = 5$ Volts

Voltage in 6Ω Resistor = $6 * 1 = 6$ Volts

Voltage in 4Ω Resistor = $4 * 1 = 4$ Volts

Voltage in 10Ω Resistor = 0 Volts

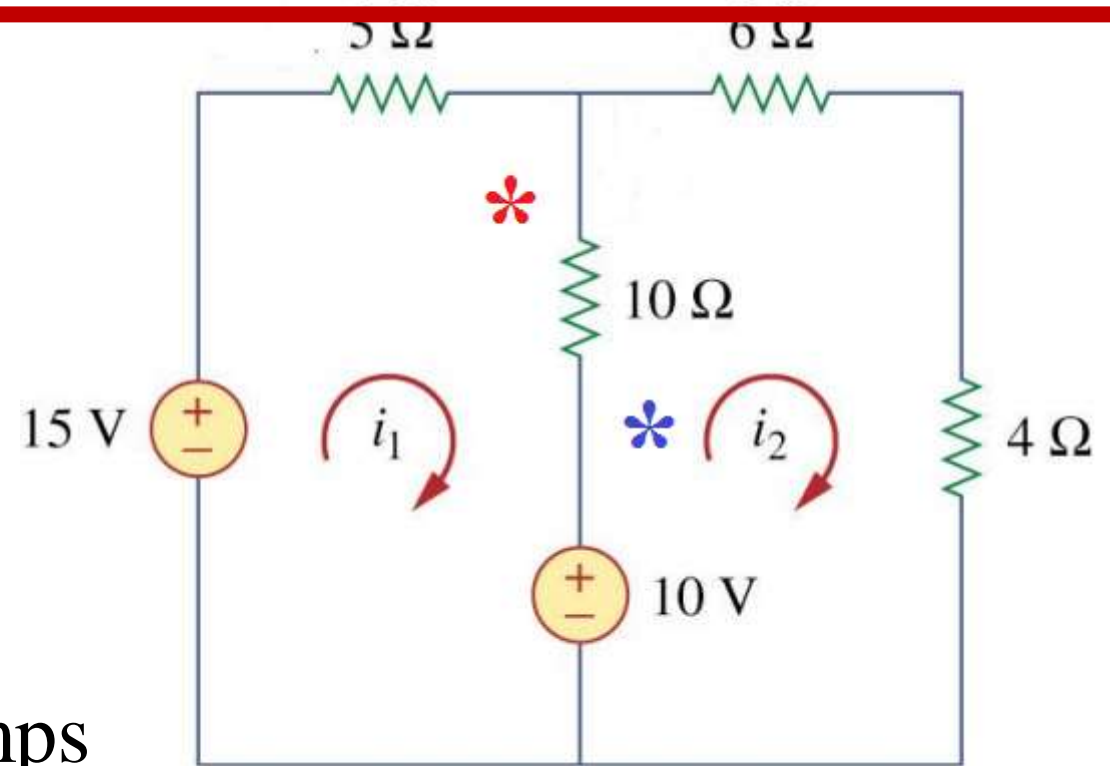

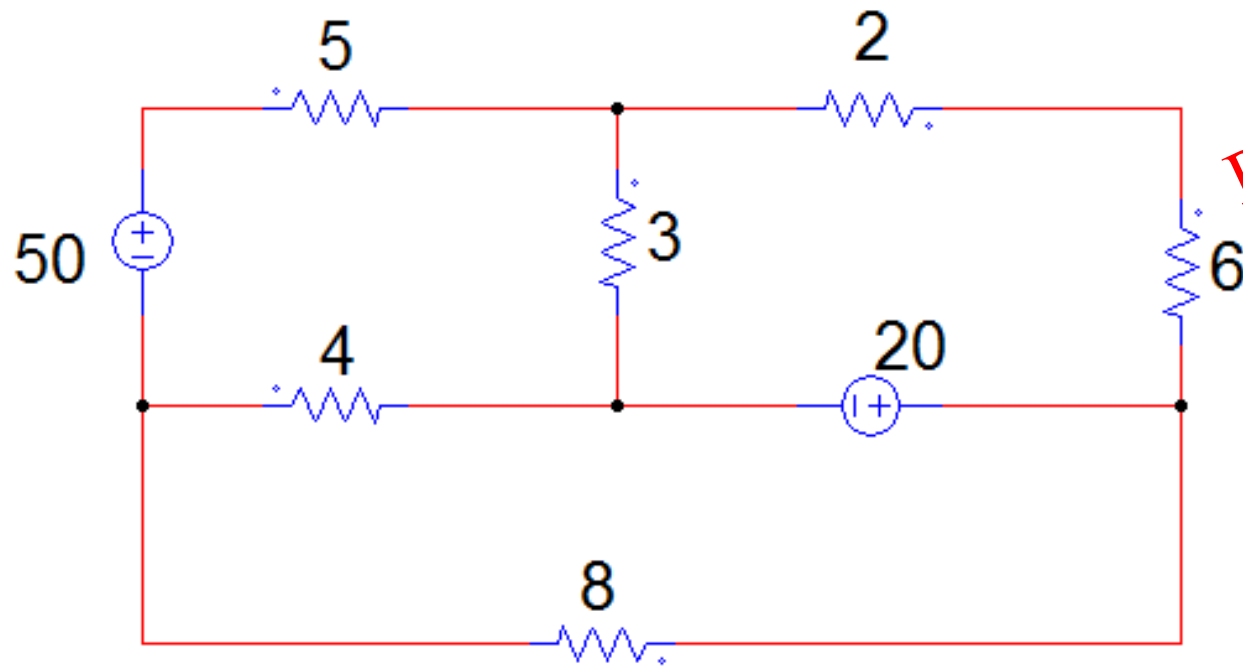

Problem No.2


Solve the given circuit by Mesh Analysis and find the loop currents

Solution for Problem No.2

$$R_{11} = 5 + 3 + 4 = 12$$

$$R_{22} = 2 + 6 + 3 = 11$$

$$R_{33} = 4 + 8 = 12$$

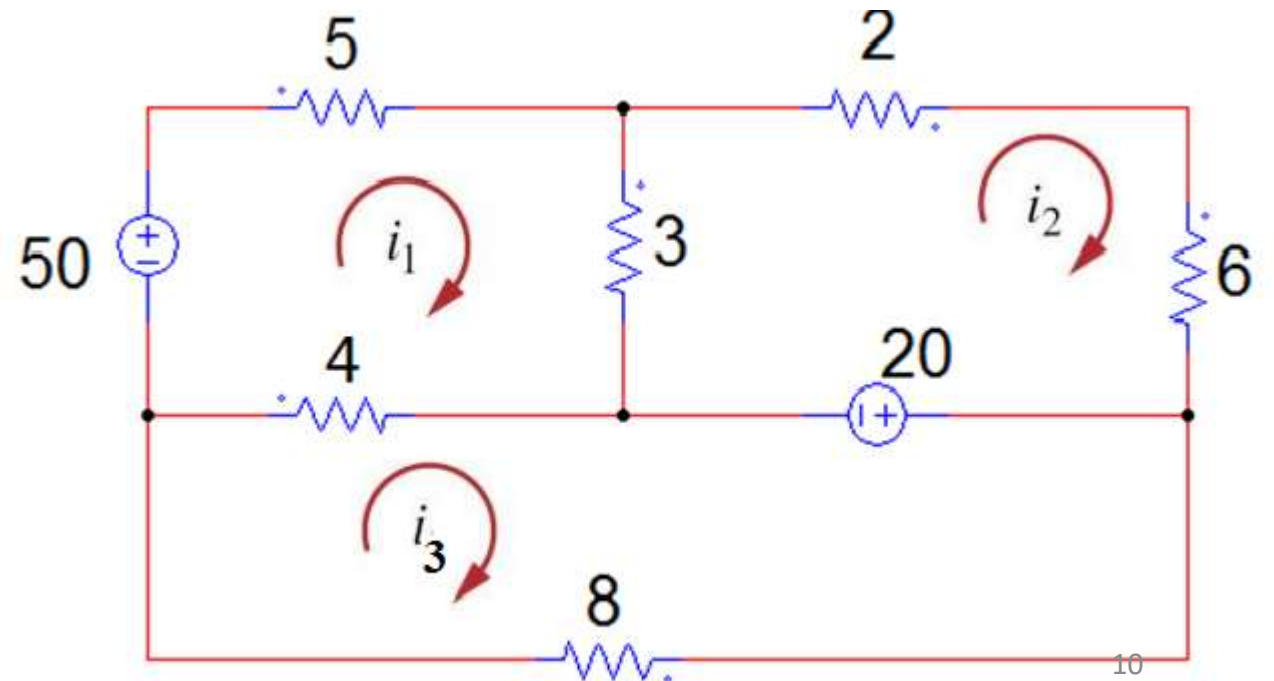

Solution for Problem No.2

$$R_{12}=R_{21}= -3$$

$$R_{13}=R_{31}= -4$$


$$R_{23}=R_{32}= 0$$

$$V_1= 50$$

$$V_2= -20$$

$$V_3=20$$
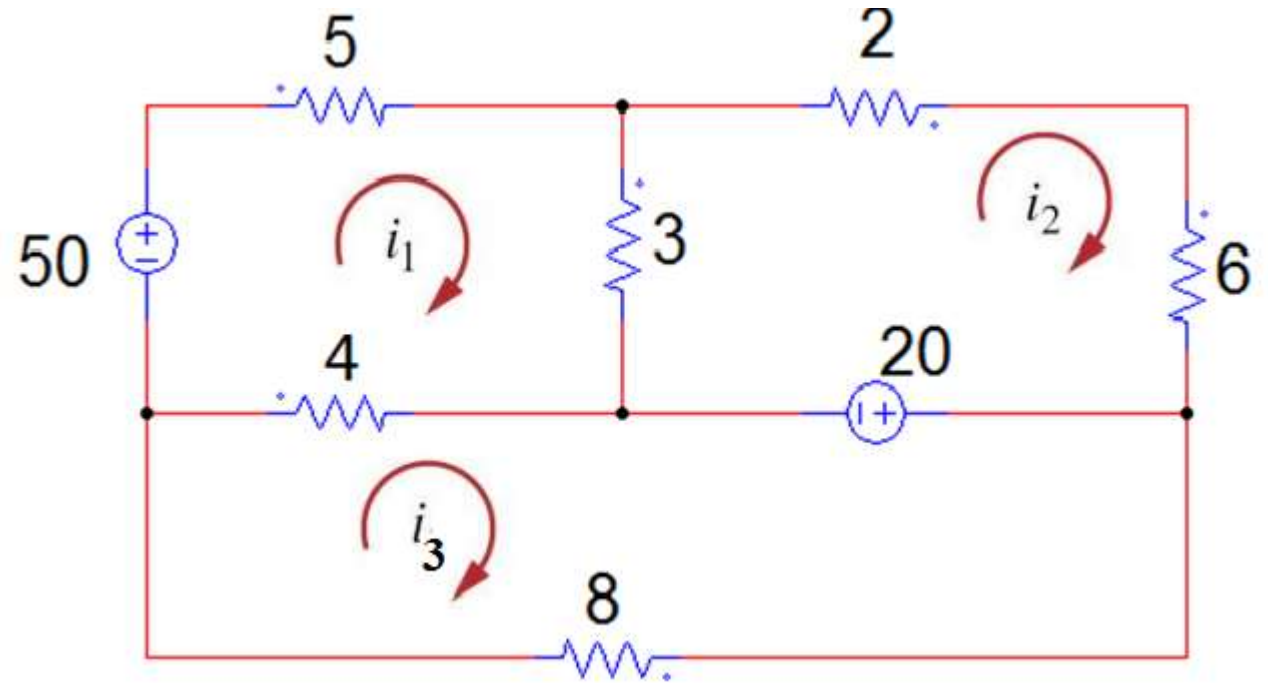
$$\begin{bmatrix} 12 & -3 & -4 \\ -3 & 11 & 0 \\ -4 & 0 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ -20 \\ 20 \end{bmatrix}$$



Solution for Problem No.2

$$\begin{bmatrix} 12 & -3 & -4 \\ -3 & 11 & 0 \\ -4 & 0 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ -20 \\ 20 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{6760}{1300} = 5.2 \text{ Amps}$$

$$\Delta = \begin{bmatrix} 12 & -3 & -4 \\ -3 & 11 & 0 \\ -4 & 0 & 12 \end{bmatrix} = 1300$$

$$\Delta_2 = \begin{bmatrix} 12 & 50 & -4 \\ -3 & -20 & 0 \\ -4 & 20 & 12 \end{bmatrix} = -520$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-520}{1300} = -0.4 \text{ Amps}$$


$$\Delta_1 = \begin{bmatrix} 50 & -3 & -4 \\ -20 & 11 & 0 \\ 20 & 0 & 12 \end{bmatrix} = 6760$$


$$\Delta_3 = \begin{bmatrix} 12 & -3 & 50 \\ -3 & 11 & -20 \\ -4 & 0 & 20 \end{bmatrix} = 4420$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{4420}{1300} = 3.4 \text{ Amps}$$

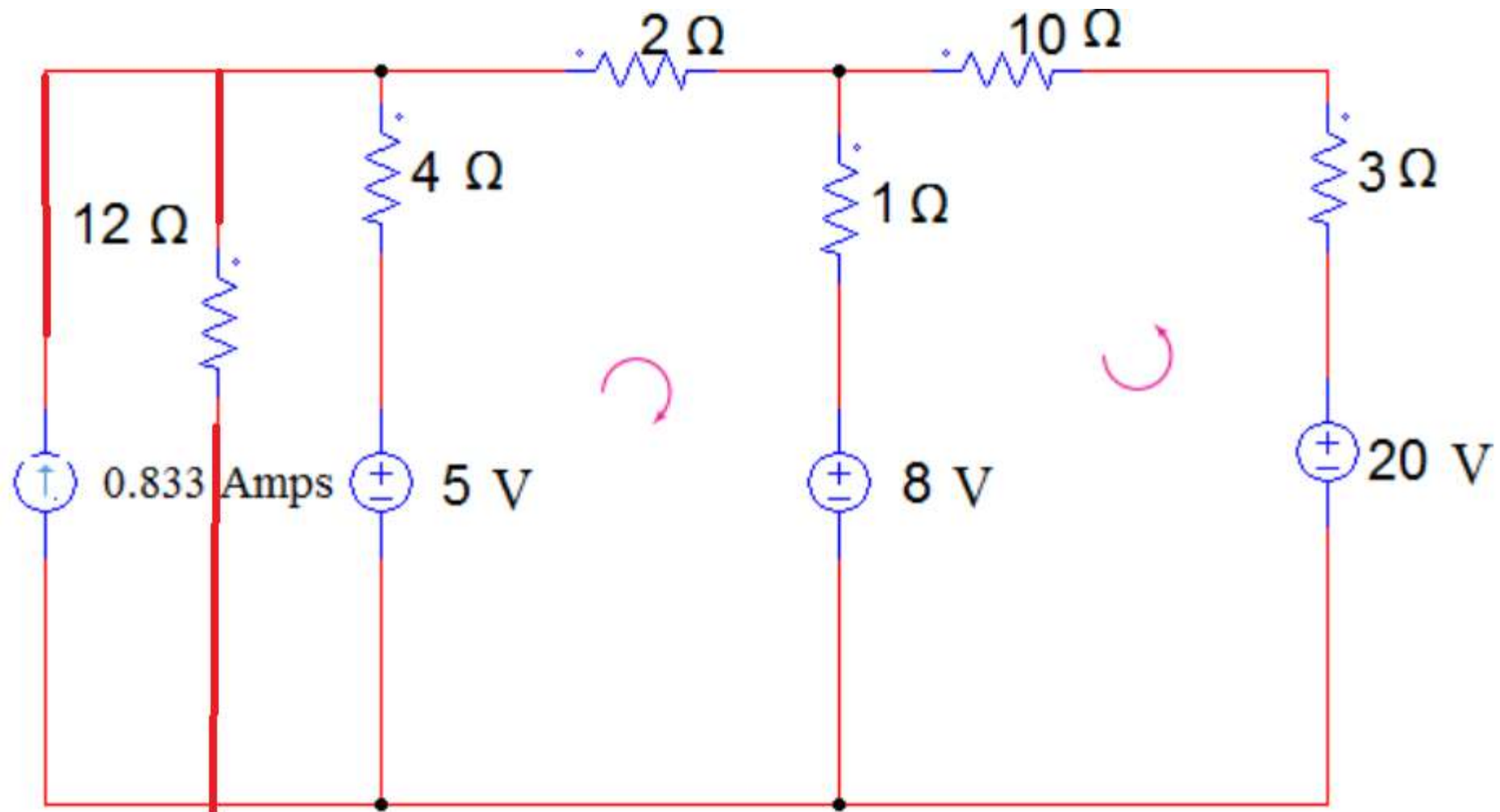Problem No.3

Find the mesh currents by using mesh analysis



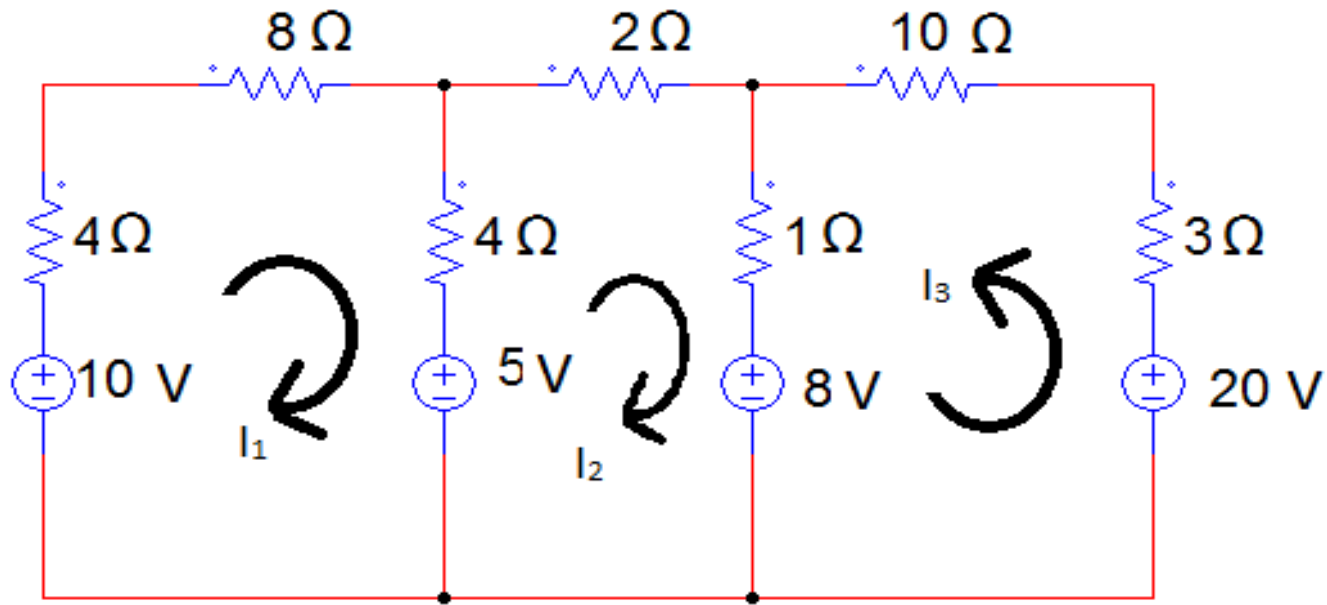

Find the mesh currents
by using mesh analysis

$$R_{11} = 4 + 8 + 4 = 16$$

$$R_{22} = 4 + 2 + 1 = 7$$

$$R_{33} = 1 + 10 + 3 = 14$$

$$R_{12} = R_{21} = -4$$

$$R_{23} = R_{32} = 1$$

$$R_{13} = R_{31} = 0$$

$$V_1 = 10 - 5 = 5$$

$$V_2 = 5 - 8 = -3$$

$$V_3 = -8 + 20 = 12$$

$$\begin{bmatrix} 16 & -4 & 0 \\ -4 & 7 & 1 \\ 0 & 1 & 14 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ -3 \\ 12 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 16 & -4 & 0 \\ -4 & 7 & 1 \\ 0 & 1 & 14 \end{bmatrix} = 1328$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{269}{1328} = 0.2026 \text{Amps}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-584}{1328} = -0.4398 \text{Amps}$$





$$\Delta_1 = \begin{bmatrix} 5 & -4 & 0 \\ -3 & 7 & 1 \\ 12 & 1 & 14 \end{bmatrix} = 269$$

$$\Delta_2 = \begin{bmatrix} 16 & 5 & 0 \\ -4 & -3 & 1 \\ 0 & 12 & 14 \end{bmatrix} = -584$$



$$\Delta_3 = \begin{bmatrix} 16 & -4 & 5 \\ -4 & 7 & -3 \\ 0 & 1 & 12 \end{bmatrix} = 1180$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{1180}{1328} = 0.886 \text{Amps}$$

Additional problems

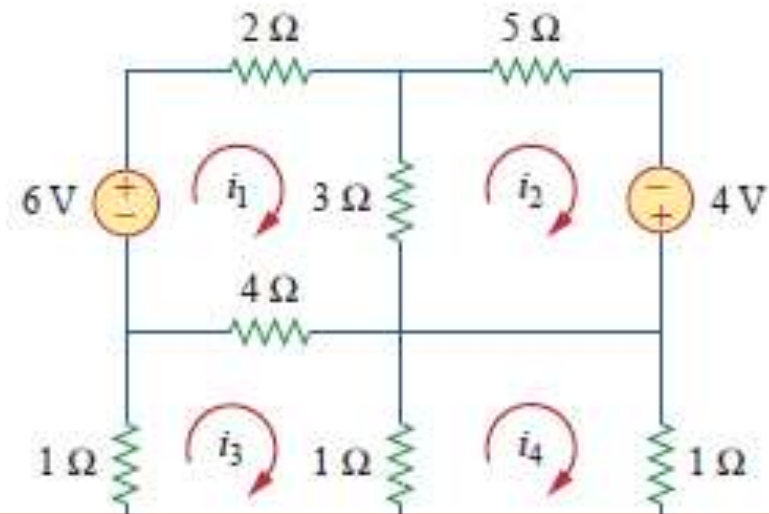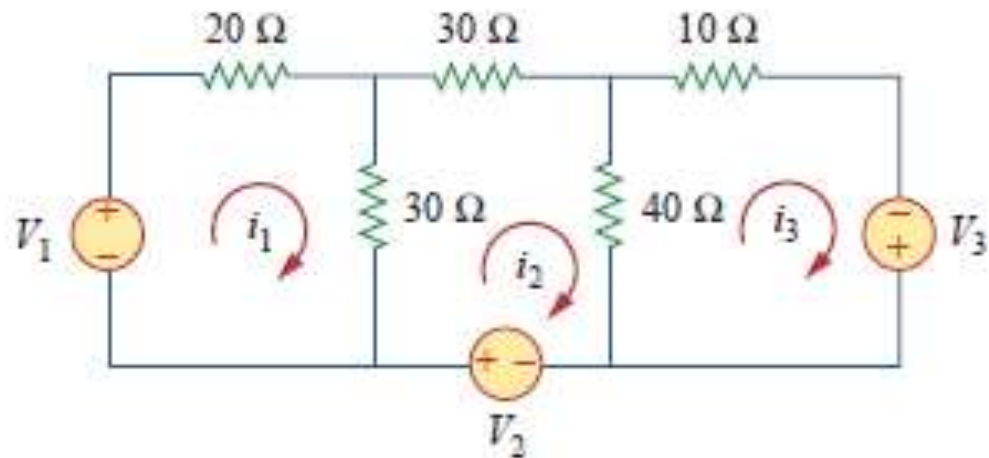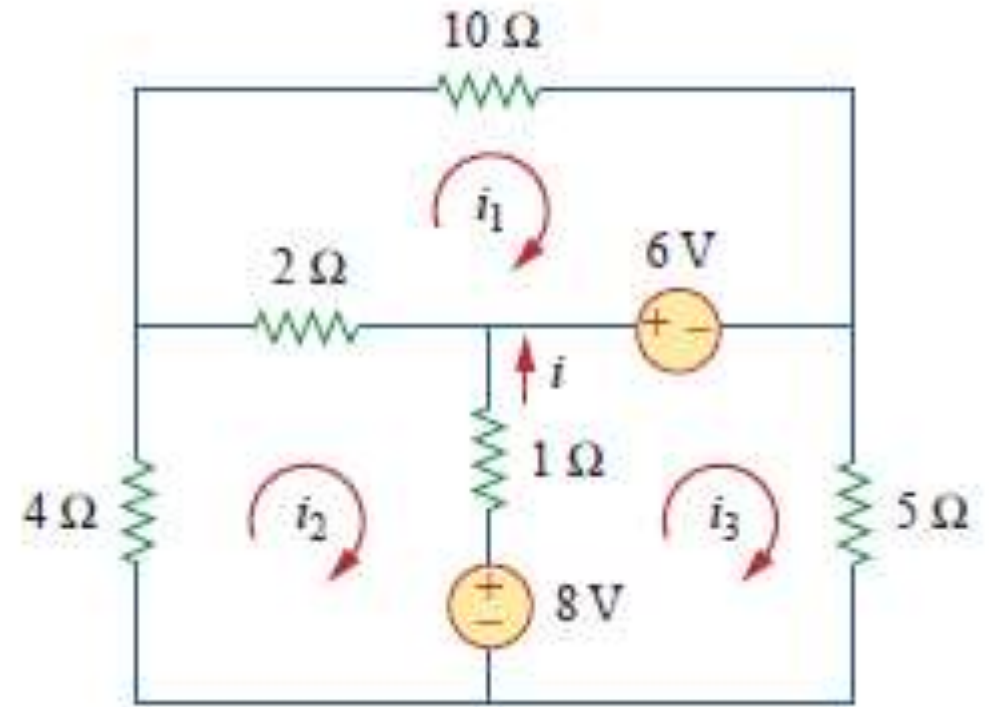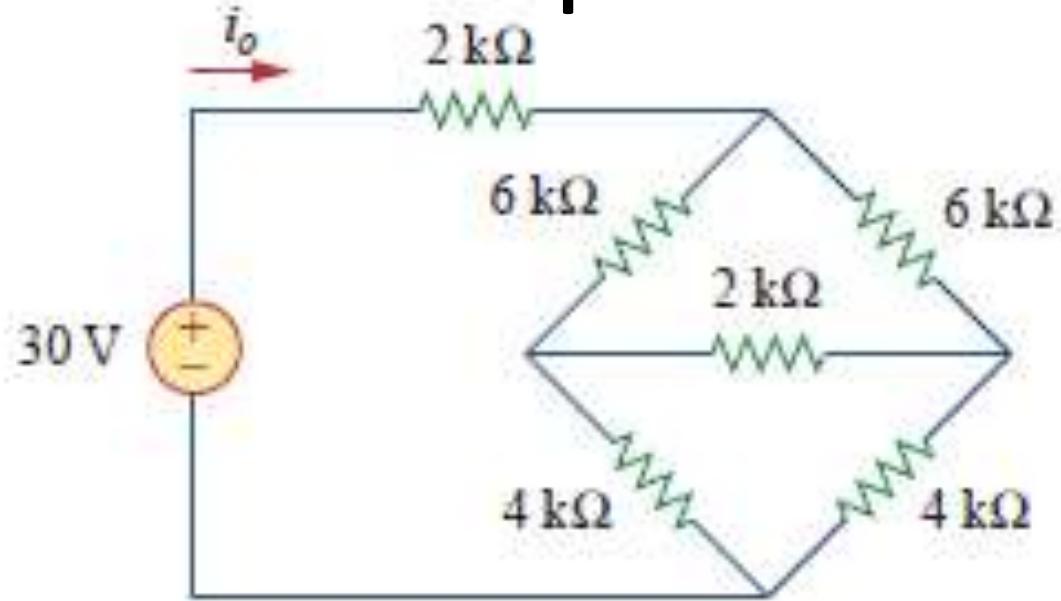


Additional problems

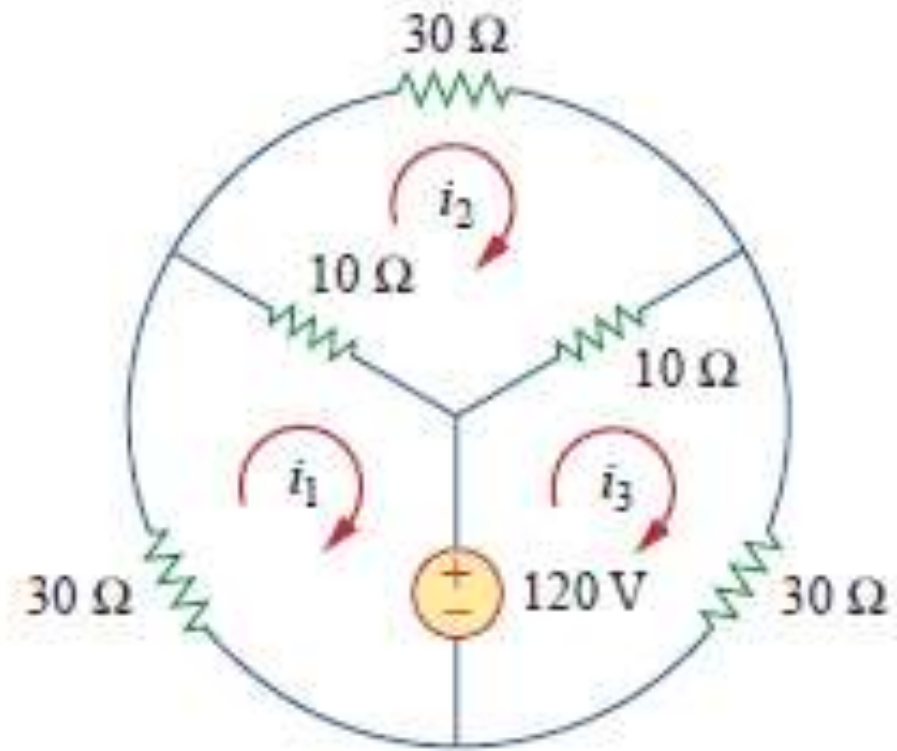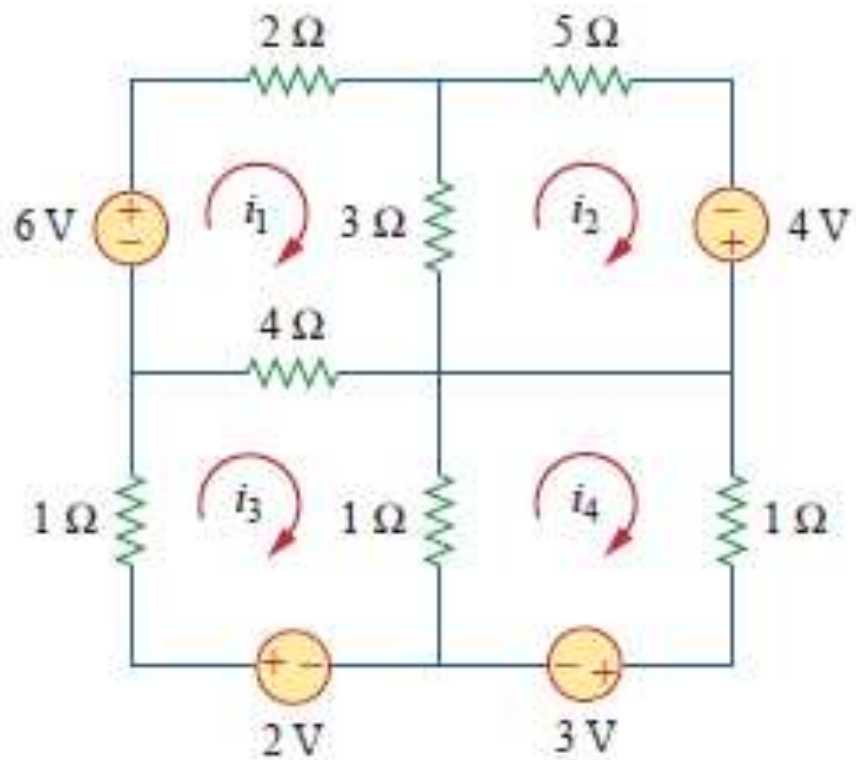

Nodal Analysis Concept



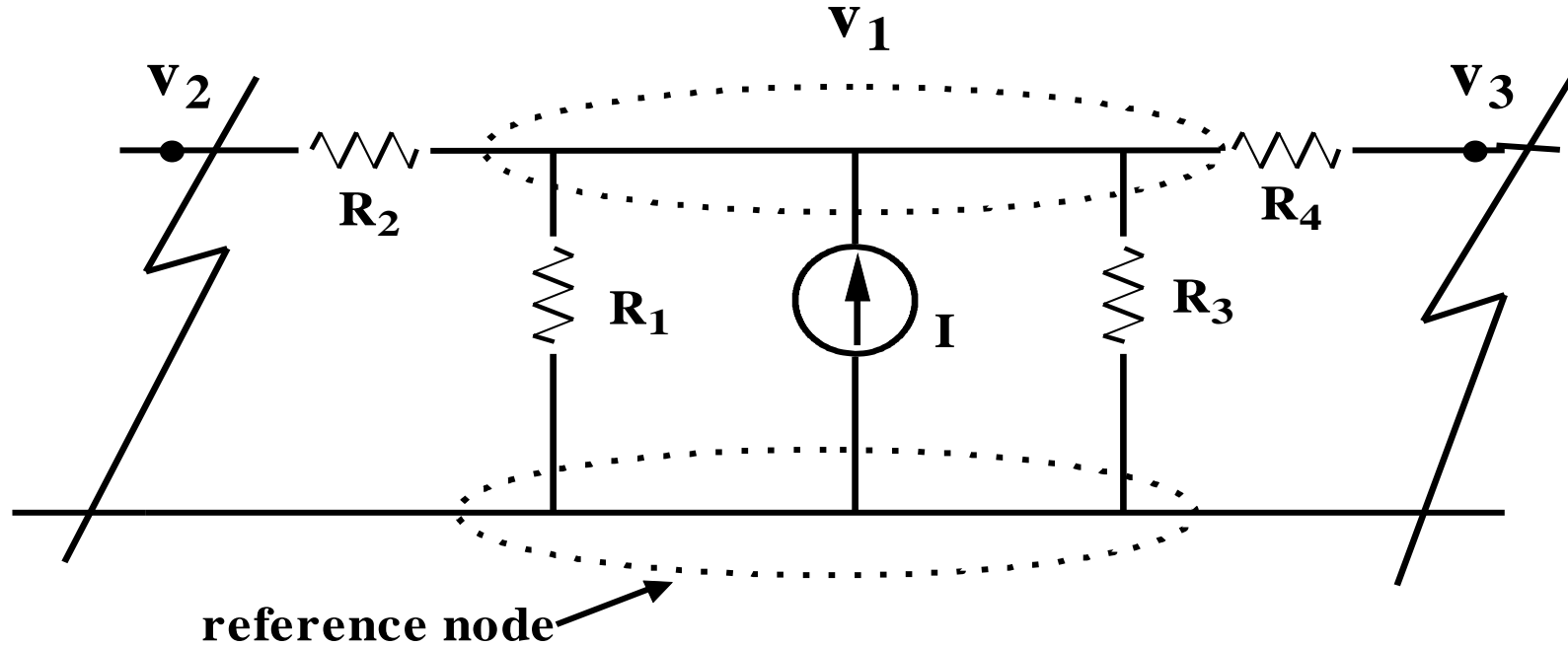
Three or more elements joined together is called as Node.



$$\frac{V_1 - V_2}{R_2} + \frac{V_1}{R_1} + \frac{V_1}{R_3} + \frac{V_1 - V_3}{R_4} = I$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) V_1 - \left(\frac{1}{R_2} \right) V_2 - \left(\frac{1}{R_4} \right) V_3 = I$$

Identify the number of nodes

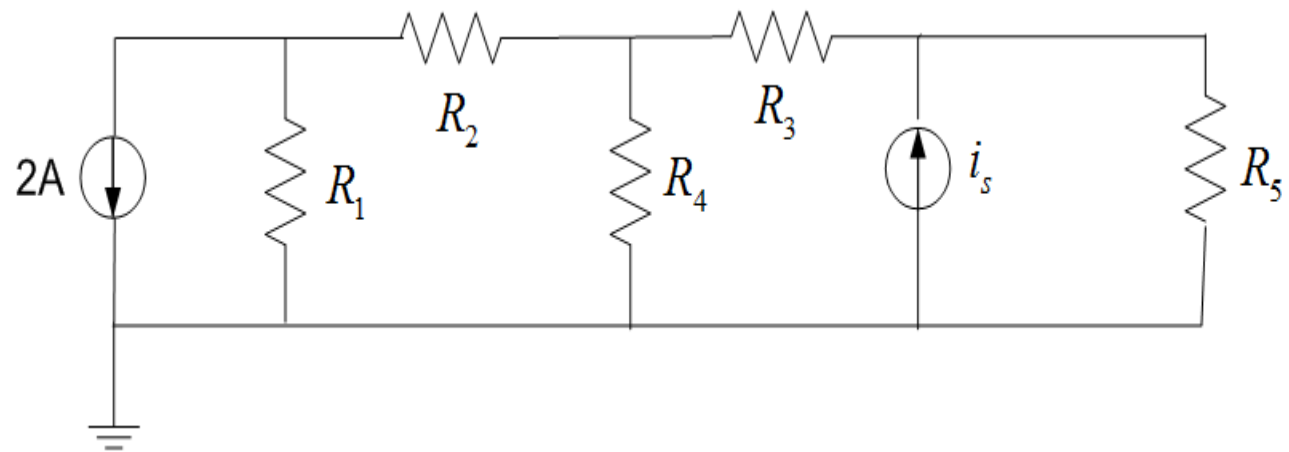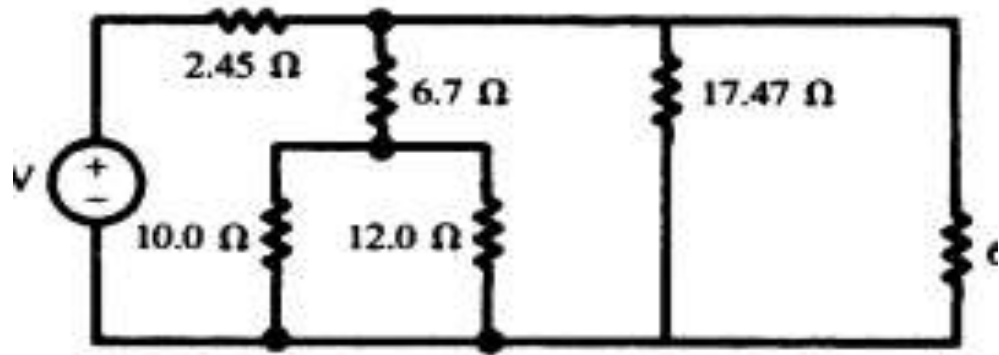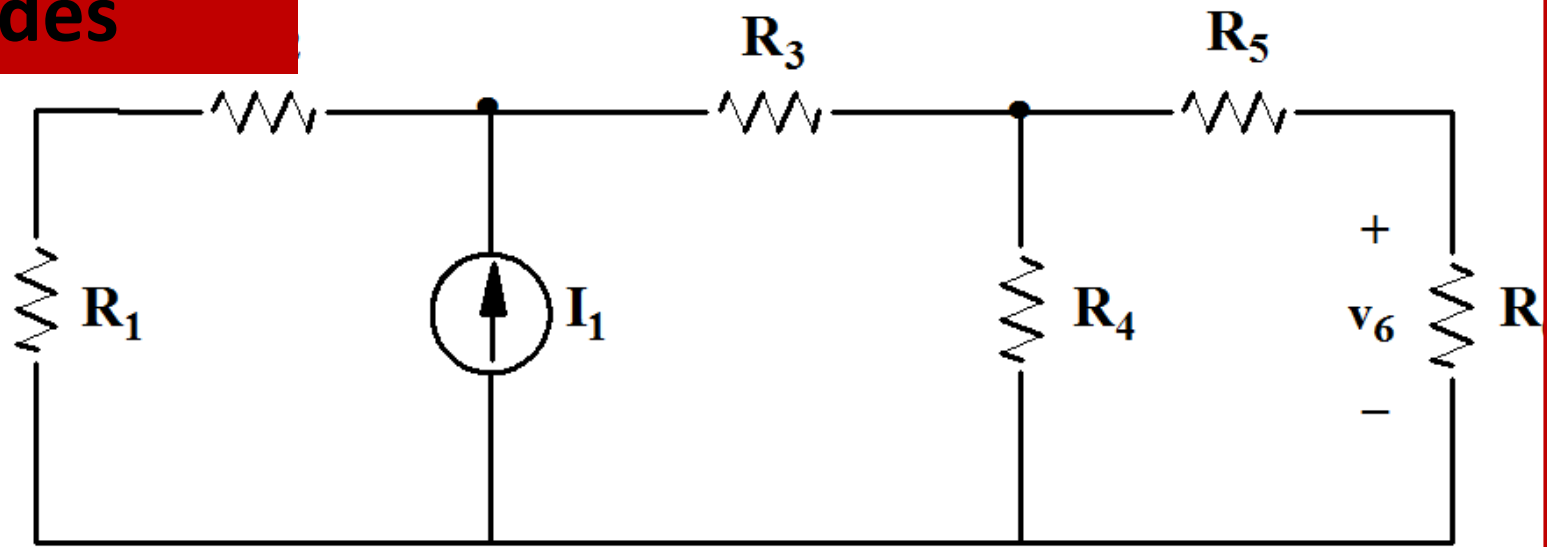







Nodal Analysis by Inspection method

If the circuit contains 2 major nodes then matrix will be 2X2 matrix

$$\begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Where

- G_{11}  Sum of the conductance's in node No. 1
- G_{22}  Sum of the conductance's in node No. 2
- G_{33}  Sum of the conductance's in node No. 3
- $G_{31} = G_{13}$  Sum of the conductance's connected between node No. 1 and 3
- $G_{12} = G_{21}$  Sum of the conductance's connected between node No. 1 and 2
- $G_{32} = G_{23}$  Sum of the conductance's connected between node No. 2 and 3







By ohms law $V=IR$

$$I=1/R * V$$

$$I=GV$$

If the circuit contains 3 major nodes then matrix will be 3X3 matrix

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

- I_1  Sum of the currents flowing towards node no. 1
- I_2  Sum of the currents flowing towards node no. 2
- I_3  Sum of the currents flowing towards node no.3
- V_1  Unknown node voltage of node no. 1
- V_2  Unknown node voltage of node no. 2
- V_3  Unknown node voltage of node no. 3

Rules:

All the diagonal(G_{11}, G_{22}, G_{33}) elements are positive.


All the Non diagonal($G_{12}, G_{13}, G_{23}, G_{32}, G_{21}, G_{31}$) elements are negative.

Note:

For inspection method the circuit should contain only current source. If voltage source is present convert it into current source and then apply inspection method.

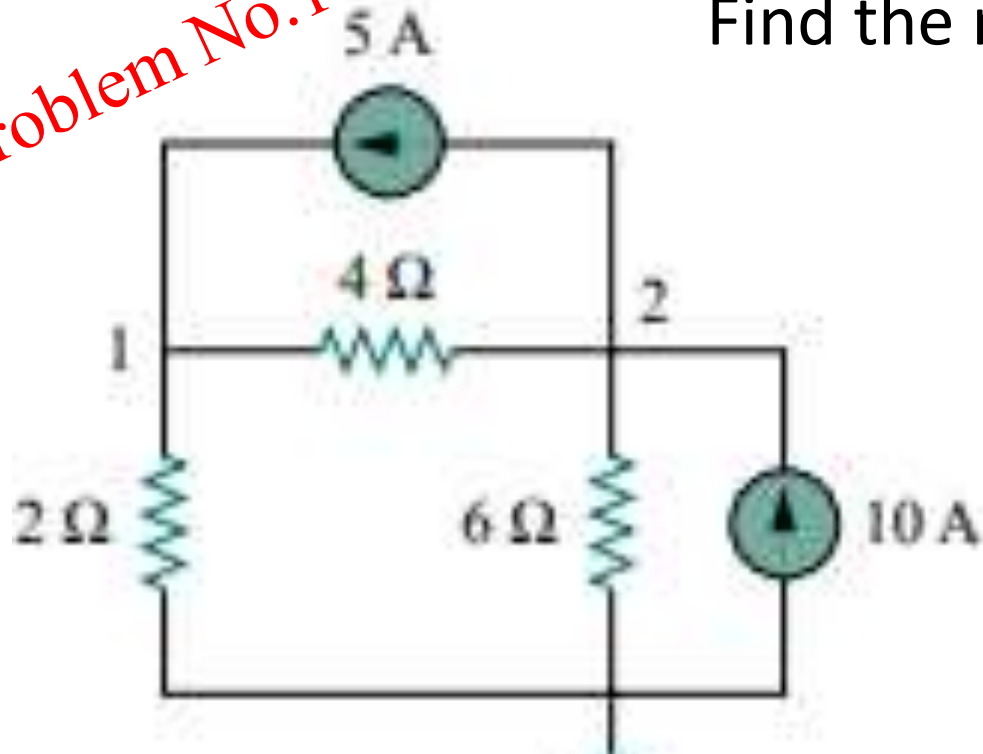Problem No.1

Find the node voltages and branch currents.



Since there are 2 nodes we have 2x2 matrix

$$\begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$G_{11} = \frac{1}{2} + \frac{1}{4} = 0.25 + 0.5 = 0.75$$

$$G_{22} = \frac{1}{4} + \frac{1}{6} = 0.25 + 0.1666 = 0.4166$$

$$G_{12} = G_{21} = \frac{1}{4} = 0.25 = -0.25$$

$$I_1 = 5$$

$$I_2 = -5 + 10 = 5$$

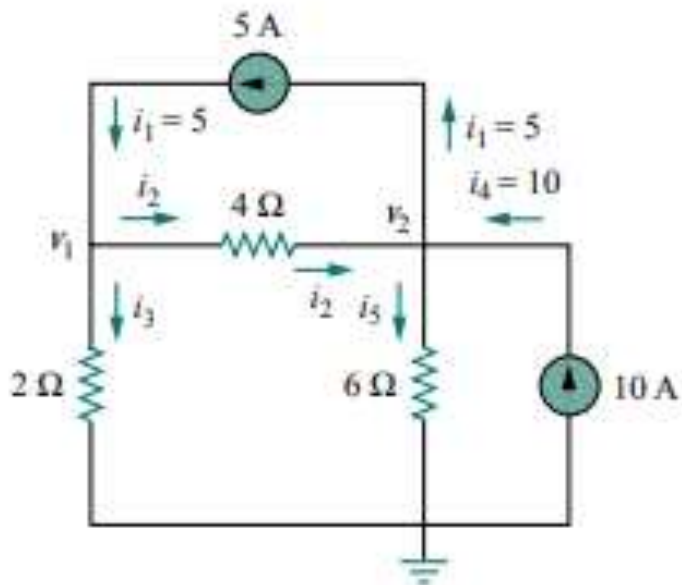

$$\begin{bmatrix} 0.75 & -0.25 \\ -0.25 & 0.4166 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

$$\begin{bmatrix} 0.75 & -0.25 \\ -0.25 & 0.4166 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 0.75 & -0.25 \\ -0.25 & 0.4166 \end{bmatrix} = 0.24995$$

$$\Delta_1 = \begin{bmatrix} 5 & -0.25 \\ 5 & 0.4166 \end{bmatrix} = 3.333$$

$$\Delta_2 = \begin{bmatrix} 0.75 & 5 \\ -0.25 & 5 \end{bmatrix} = 5$$

$$V_1 = \frac{\Delta_1}{\Delta} = 13.33 \text{ Volts}$$

$$V_2 = \frac{\Delta_2}{\Delta} = 20 \text{ Volts}$$


$$I_{2\Omega} = \frac{V_1}{2} = 6.665 \text{ Amps}$$

$$I_{4\Omega} = \frac{V_2 - V_1}{4} = 1.6675 \text{ Amps}$$


$$I_{6\Omega} = \frac{V_2}{6} = 3.33 \text{ Amps}$$

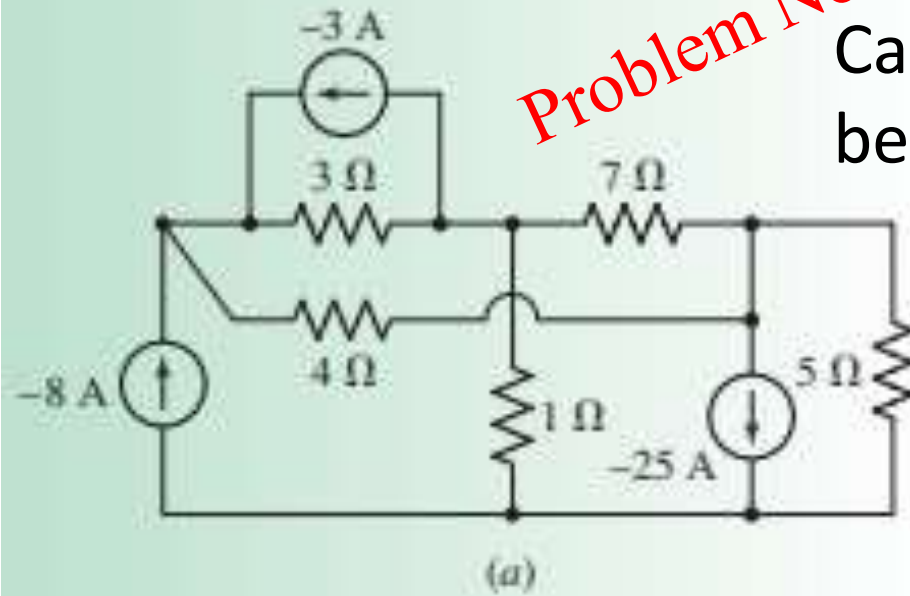Problem No.2


Calculate the node voltages for the circuit given below



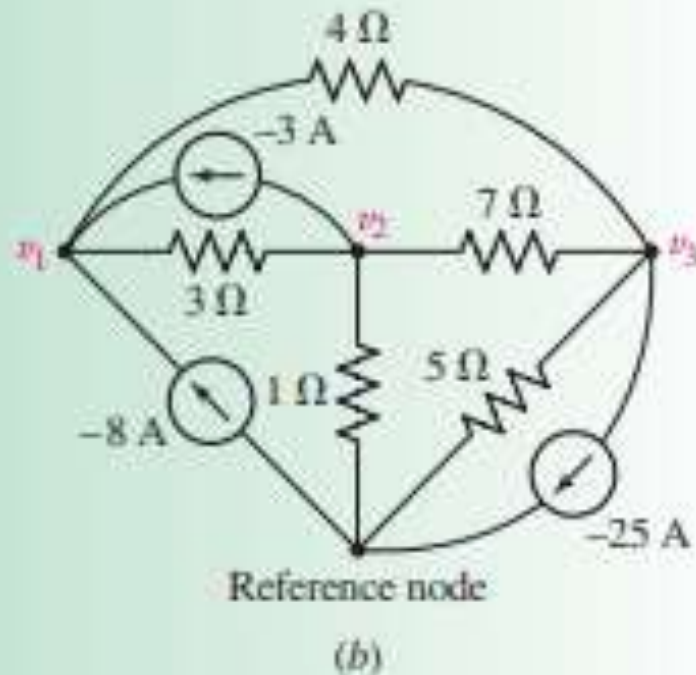
SOLUTION: Since there are three nodes we have 3x3 matrix


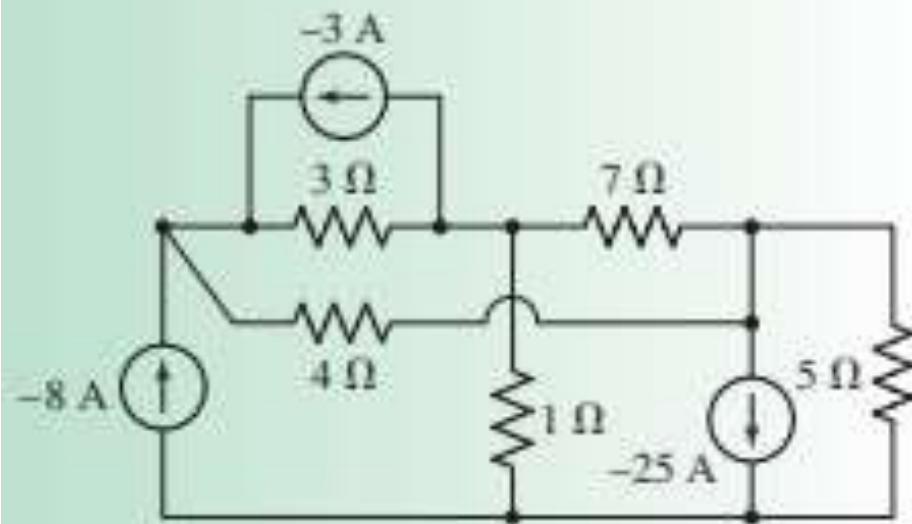
$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$



(a)

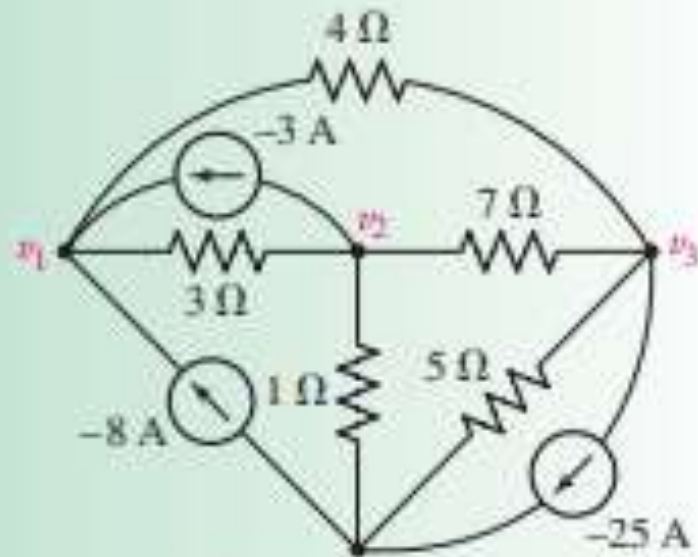

Reference node

(b)

$$G_{11} = \frac{1}{3} + \frac{1}{4} = 0.5833$$

$$G_{22} = \frac{1}{3} + \frac{1}{1} + \frac{1}{7} = 1.4762$$

$$G_{33} = \frac{1}{5} + \frac{1}{7} + \frac{1}{4} = 0.5929$$

$$G_{13} = G_{31} = \frac{1}{4} = 0.25$$

$$I_1 = -3 - 8 = -11$$

$$I_2 = -(-3) = 3$$

$$I_3 = -(-25) = 25$$

$$G_{12} = G_{21} = \frac{1}{3} = 0.33$$

$$G_{32} = G_{23} = \frac{1}{7} = 0.1429$$

$$\begin{bmatrix} 0.5833 & -0.33 & -0.25 \\ -0.33 & 1.4762 & -0.1429 \\ -0.25 & -0.1429 & 0.5929 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix}$$

$$v_1 = \frac{\begin{vmatrix} -11 & -0.3333 & -0.2500 \\ 3 & 1.4762 & -0.1429 \\ 25 & -0.1429 & 0.5929 \end{vmatrix}}{\begin{vmatrix} 0.5833 & -0.3333 & -0.2500 \\ -0.3333 & 1.4762 & -0.1429 \\ -0.2500 & -0.1429 & 0.5929 \end{vmatrix}} = \frac{1.714}{0.3167} = 5.412 \text{ V}$$

Similarly,


$$v_2 = \frac{\begin{vmatrix} 0.5833 & -11 & -0.2500 \\ -0.3333 & 3 & -0.1429 \\ -0.2500 & 25 & 0.5929 \end{vmatrix}}{0.3167} = \frac{2.450}{0.3167} = 7.736 \text{ V}$$

and

$$v_3 = \frac{\begin{vmatrix} 0.5833 & -0.3333 & -11 \\ -0.3333 & 1.4762 & 3 \\ -0.2500 & -0.1429 & 25 \end{vmatrix}}{0.3167} = \frac{14.67}{0.3167} = 46.32 \text{ V}$$

$$\begin{bmatrix} 0.5833 & -0.33 & -0.25 \\ -0.33 & 1.4762 & -0.1429 \\ -0.25 & -0.1429 & 0.5929 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix}$$

Problem No.3

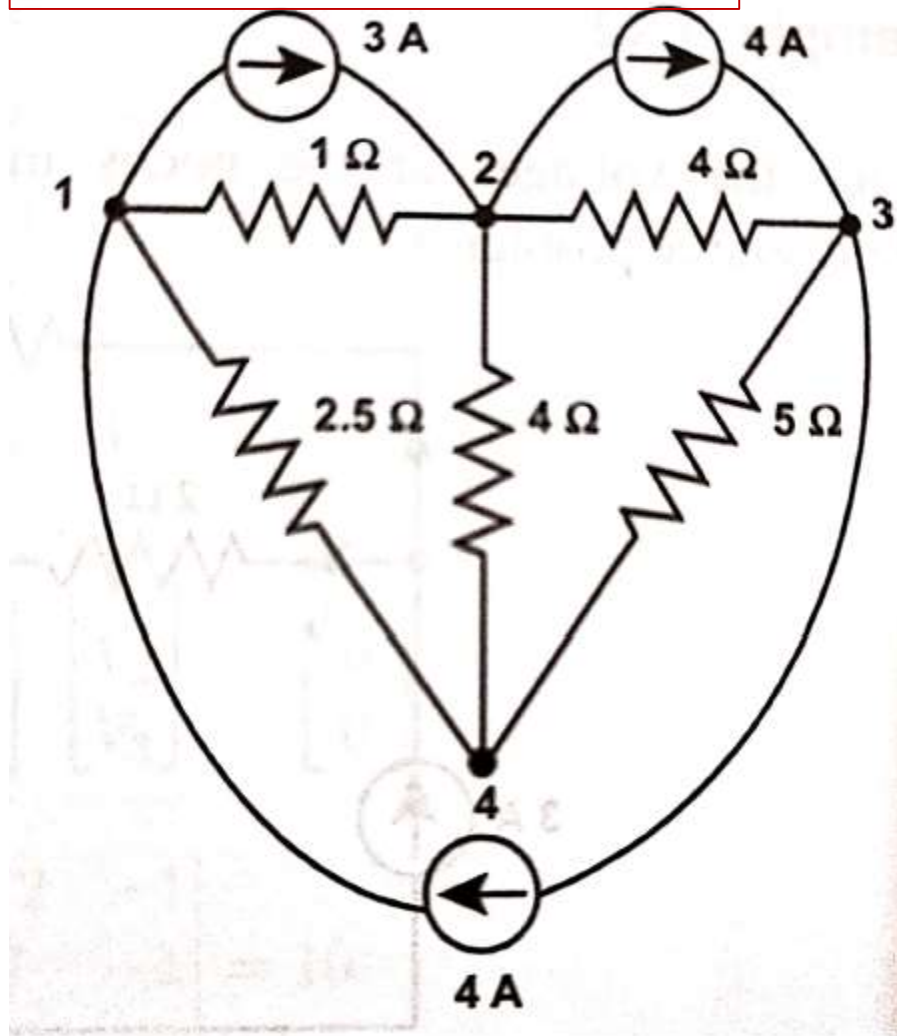

Find the voltage across the node 2 and 4 by nodal analysis

$$G_{11} = \frac{1}{1} + \frac{1}{2.5} = 1.4$$

$$G_{22} = \frac{1}{4} + \frac{1}{1} + \frac{1}{4} = 1.5$$

$$G_{33} = \frac{1}{4} + \frac{1}{5} = 0.45$$

$$G_{13} = G_{31} = 0$$

$$G_{12} = G_{21} = \frac{1}{1} = 1 = -1$$

$$G_{32} = G_{23} = \frac{1}{4} = 0.25 = -0.25$$

$$I_1 = 4 - 3 = 1$$

$$I_2 = 3 - 4 = -1$$

$$I_3 = 4 - 4 = 0$$

$$\begin{bmatrix} 1.4 & -1 & 0 \\ -1 & 1.5 & -0.25 \\ 0 & -0.25 & 0.45 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \\ 0 \end{bmatrix}$$


$$\Delta_2 = \begin{bmatrix} 1.4 & 1 & 0 \\ -1 & -1 & -0.25 \\ 0 & 0 & 0.45 \end{bmatrix} = -0.28$$

$$\Delta = \begin{bmatrix} 1.4 & -1 & 0 \\ -1 & 1.5 & -0.25 \\ 0 & -0.25 & 0.45 \end{bmatrix} = 0.665$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-0.28}{0.665} = -0.421 \text{ Volts}$$

$$V_{4\Omega} = V_2 - V_4 = -0.421 - 0 = -0.421 \text{ Volts}$$

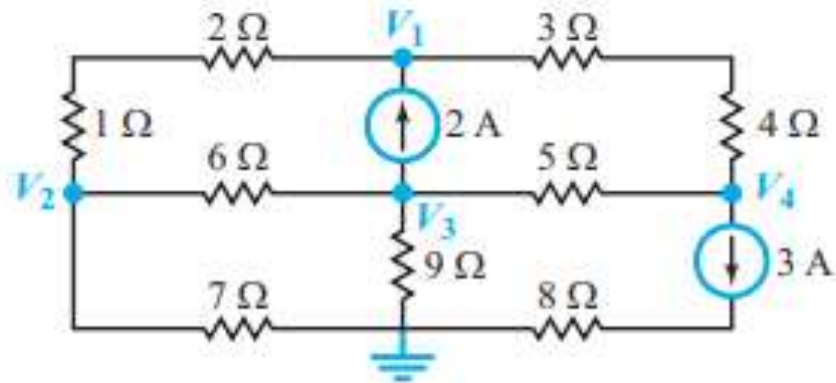Use the by-inspection method to establish a node-voltage matrix equation for the circuit to find V_1 to V_4 .



$$\begin{bmatrix} 0.476 & -0.333 & 0 & -0.143 \\ -0.333 & 0.643 & -0.167 & 0 \\ 0 & -0.167 & 0.478 & -0.2 \\ -0.143 & 0 & -0.2 & 0.343 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ -2 \\ -3 \end{bmatrix}$$

Matrix inversion gives:

$$V_1 = -8.1689 \text{ V}, \quad V_2 = -8.4235 \text{ V}, \quad V_3 = -16.155 \text{ V}, \quad V_4 = -21.5748 \text{ V}.$$

$$G_{11} = \frac{1}{2+1} + \frac{1}{3+4} = 0.476$$

$$G_{12} = G_{21} = -\frac{1}{2+1} = -0.333$$

$$G_{13} = G_{31} = 0$$

$$G_{14} = G_{41} = -\frac{1}{3+4} = -0.143$$

$$G_{22} = \frac{1}{1+2} + \frac{1}{7} + \frac{1}{6} = 0.643$$

$$G_{23} = G_{32} = -\frac{1}{6} = -0.167$$



$$G_{24} = G_{42} = 0$$


$$G_{33} = \frac{1}{5} + \frac{1}{6} + \frac{1}{9} = 0.478$$

$$G_{34} = G_{43} = -\frac{1}{5} = -0.2$$

$$G_{44} = \frac{1}{3+4} + \frac{1}{5} = 0.343$$

Additional problems

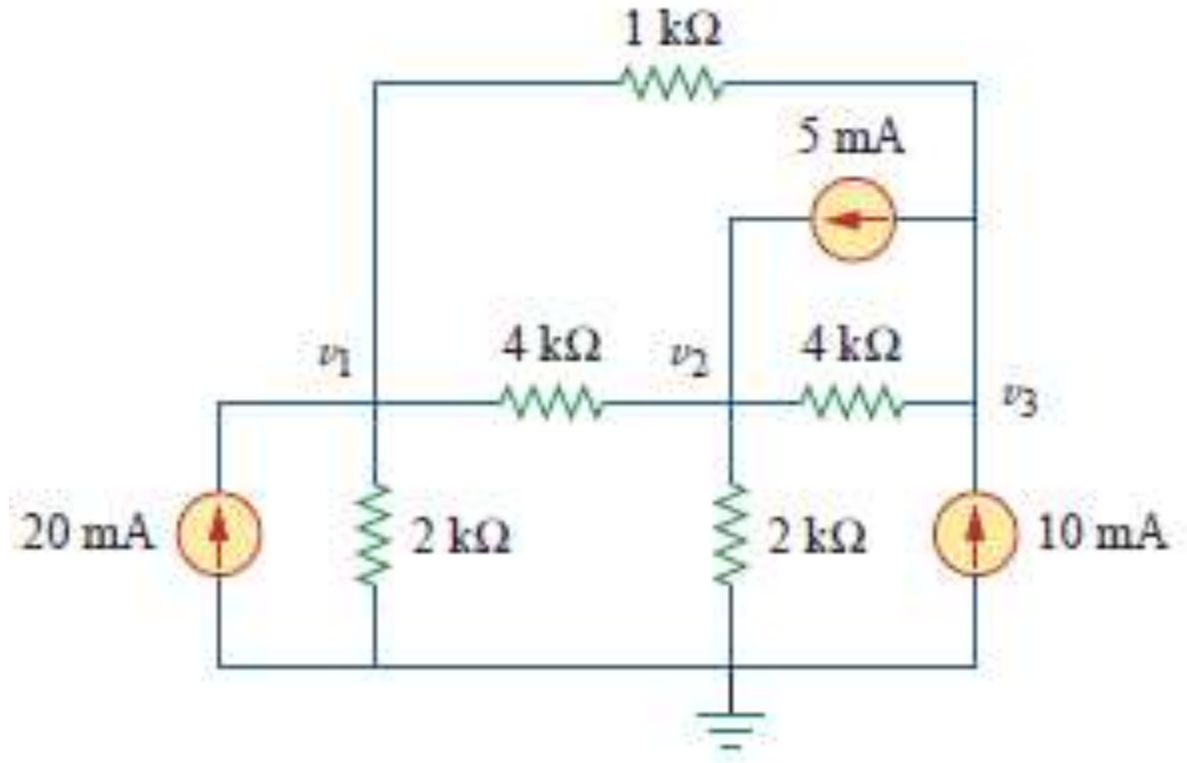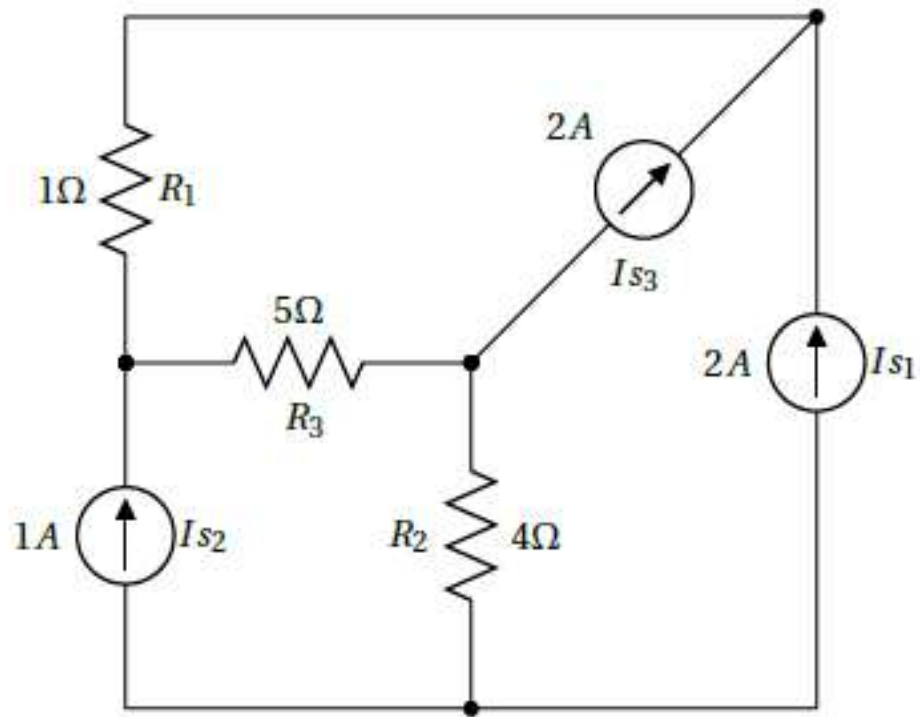

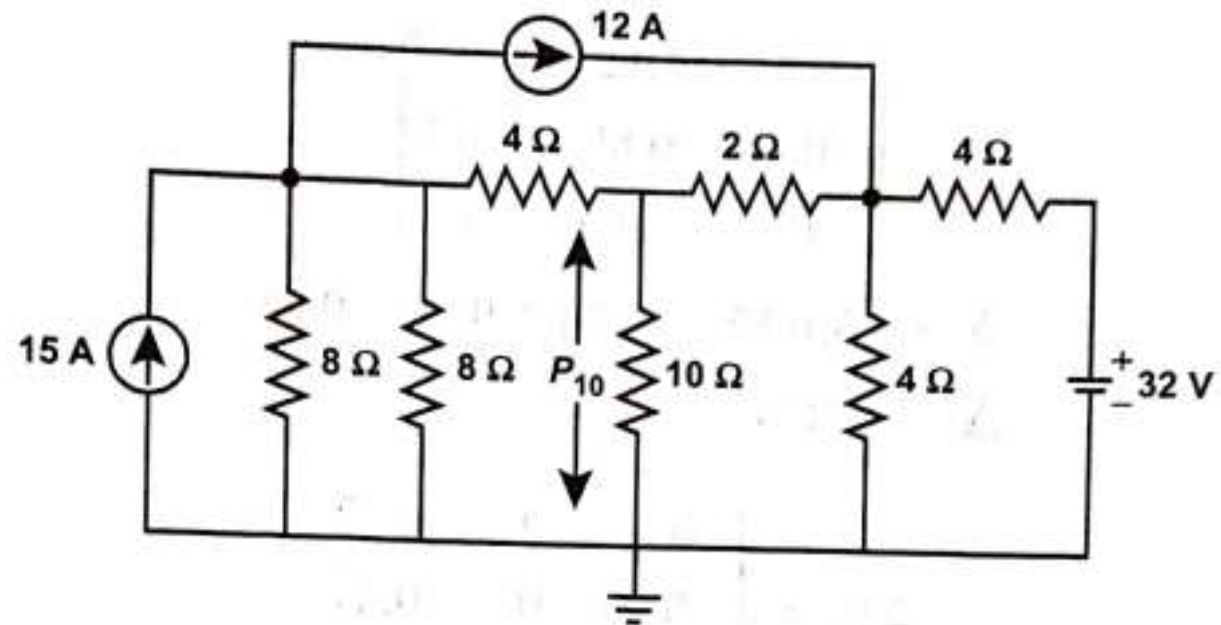

THANK YOU