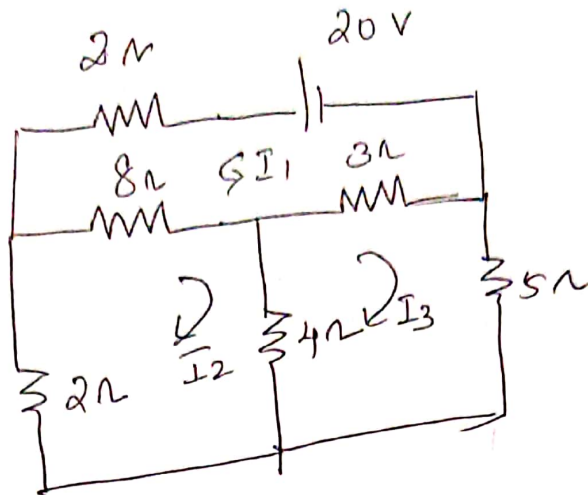



①



$$\begin{bmatrix} 13 & 8 & 3 \\ 8 & 14 & -4 \\ 3 & -4 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

Find $I_{2\Omega} = I_1 = \frac{\Delta_1}{\Delta}$

②

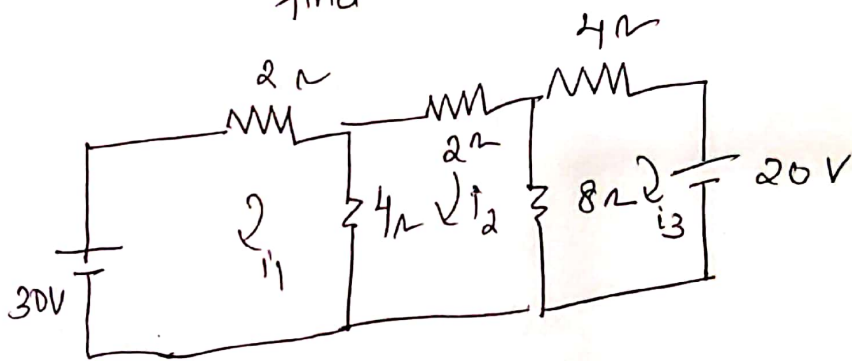


$$P_{8\Omega} = (i_8)^2 \times 8$$

$$i_8 = i_2 - i_3$$

$$\begin{bmatrix} 6 & -4 & 0 \\ -4 & 14 & -8 \\ 0 & -8 & 12 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 30 \\ 0 \\ -20 \end{bmatrix}$$

$$i_2 = \frac{\Delta_2}{\Delta}$$

$$i_3 = \frac{\Delta_3}{\Delta}$$

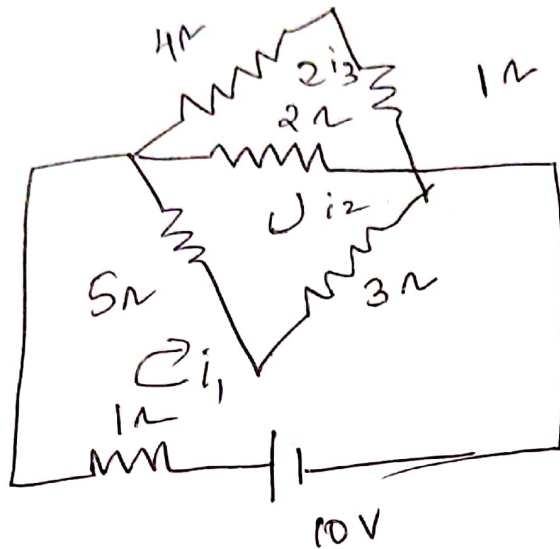

$$V_{2\Omega} = ?$$


$$V_{2\Omega} = i_{2\Omega} \times 2$$

$$\begin{pmatrix} 10 & -8 & 0 \\ -8 & 10 & -2 \\ 0 & -2 & 7 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$i_{2\Omega} = i_2 \sim i_3$$



$$i_2 = \frac{\Delta_2}{\Delta} \quad i_3 = \frac{\Delta_3}{\Delta}$$

3. Design the value of R .

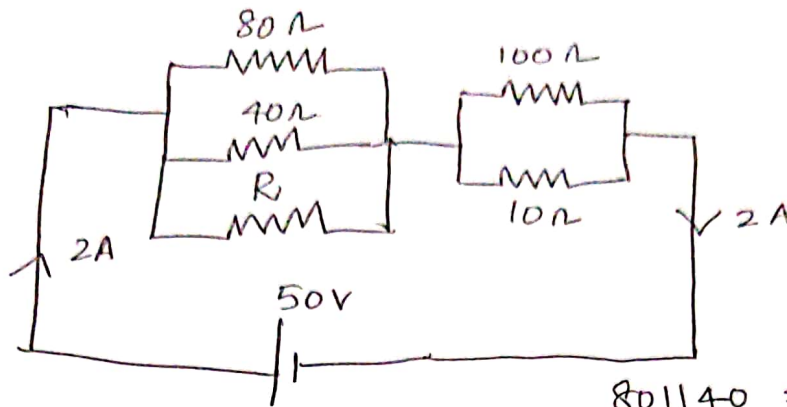

$$80 \parallel 40 = \frac{80 \times 40}{80 + 40} = 26.66$$
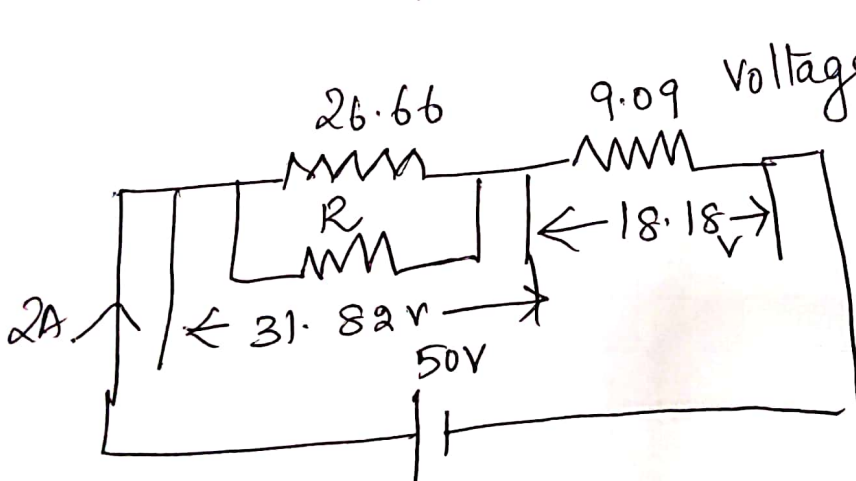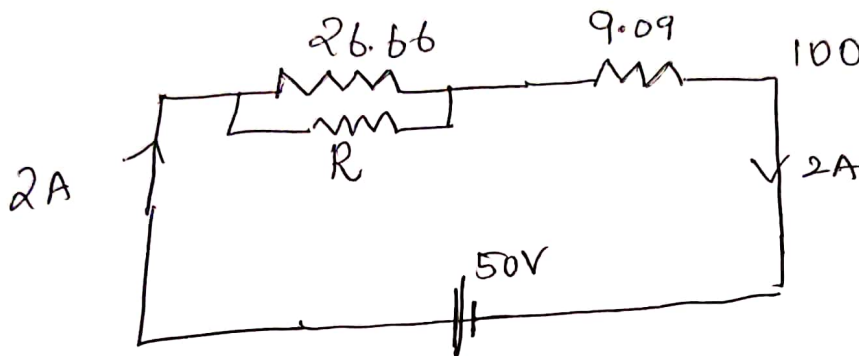
$$100 \parallel 10 = \frac{100 \times 10}{100 + 10} = 9.09$$



Voltage across 9.09

$$V = IR = 2 \times 9.09 = 18.18$$

$$50 - 18.18 = 31.82$$


$$I_{26.66} = \frac{V}{R} = \frac{31.82}{26.66} = 1.19$$

$$I_R = 2 - 1.19 = 0.81$$

$$R = \frac{V}{I} = \frac{31.82}{0.81} = 39.28$$

$$\boxed{R = 39.28}$$

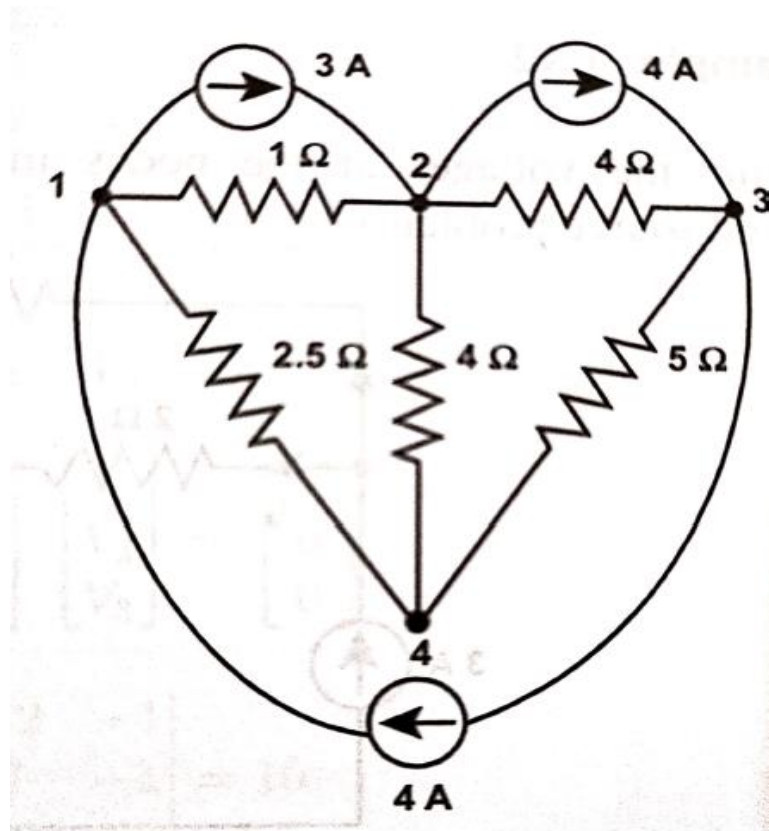5. For the given electrical circuit, estimate the voltage across 4 Ω resistances and 2.5 Ω resistance.



If the circuit contains 3 major nodes then matrix will be 3X3 matrix

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

I_1 \longrightarrow Sum of the currents flowing towards node no. 1

I_2 \longrightarrow Sum of the currents flowing towards node no. 2

I_3 \longrightarrow Sum of the currents flowing towards node no. 3

$$G_{11} = \frac{1}{1} + \frac{1}{2.5} = 1.4$$

$$G_{22} = \frac{1}{4} + \frac{1}{1} + \frac{1}{4} = 1.5$$

$$G_{33} = \frac{1}{4} + \frac{1}{5} = 0.45$$

$$G_{13} = G_{31} = 0$$

$$G_{12} = G_{21} = \frac{1}{1} = -1$$

$$G_{32} = G_{23} = \frac{1}{4} = 0.25 = -0.25$$

$$I_1 = 4 - 3 = 1$$

$$I_2 = 3 - 4 = -1$$

$$I_3 = 4 - 4 = 0$$

$$\begin{bmatrix} 1.4 & -1 & 0 \\ -1 & 1.5 & -0.25 \\ 0 & -0.25 & 0.45 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \\ 0 \end{bmatrix}$$

$$\Delta_2 = \begin{bmatrix} 1.4 & 1 & 0 \\ -1 & -1 & -0.25 \\ 0 & 0 & 0.45 \end{bmatrix} = -0.28$$

$$\Delta = \begin{bmatrix} 1.4 & -1 & 0 \\ -1 & 1.5 & -0.25 \\ 0 & -0.25 & 0.45 \end{bmatrix} = 0.665$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-0.28}{0.665} = -0.421 \text{ Volts}$$

$$V_{4\Omega} = V_2 - V_4 = -0.421 - 0 = -0.421 \text{ Volts}$$

$$V_{2.5\Omega} = V_1 - V_4$$


$$V_1 = 0.1625 / 0.665 = 0.244 \text{ Volts}$$

$$V_{2.5\Omega} = V_1 - V_4 = 0.244 - 0 = 0.244 \text{ Volts}$$

$$\text{Ans; } V_{2.5\Omega} = 0.244 \text{ Volts}$$

$$V_{4\Omega} = -0.412 \text{ Volts}$$

6. Solution:

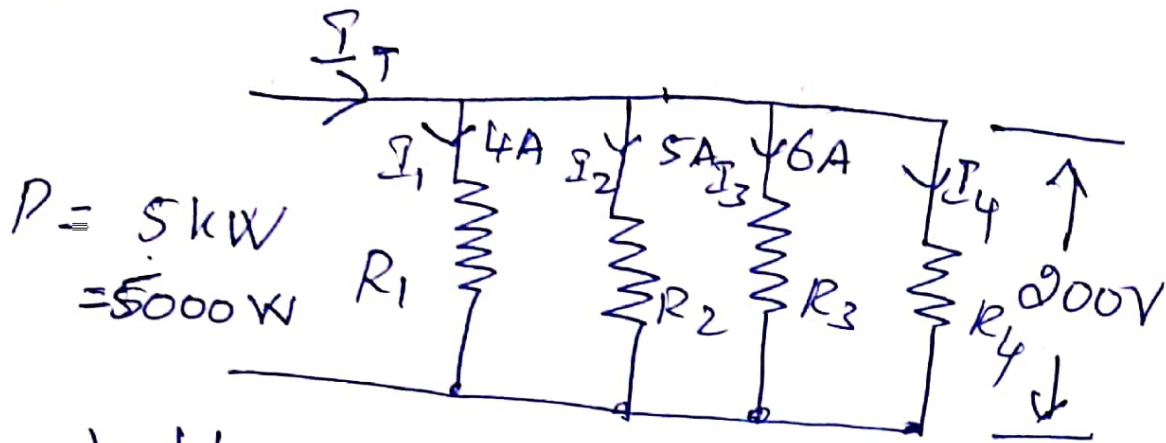

Voltage across (since $V_{R_4} = 200 \text{ V}$)
 $V_{R_1} = 200 \text{ V}$ ∴ all resistor has same voltage

$$V_{R_2} = 200 \text{ V}$$

$$V_{R_3} = 200 \text{ V}$$

$$V_T = 200 \text{ V}$$

$$P = V_T \times I_T = 200 \times I_T$$

$$I_T = P/V = \frac{5000}{200} = 25 \text{ A}$$

$$R_1 = \frac{V_{R_1}}{I_1} = \frac{200}{4 \text{ A}} ; R_2 = \frac{V_{R_2}}{I_2} = \frac{200}{5 \text{ A}} ; R_3 = \frac{V_{R_3}}{I_3} = \frac{200}{6 \text{ A}}$$

$$= \frac{200}{4}$$

$$= \frac{200}{5}$$

$$= \frac{200}{6}$$

$$R_1 = 50 \Omega$$

$$R_2 = 40 \Omega$$

$$R_3 = 33.33 \Omega$$



$$I_4 = I_T - (I_1 + I_2 + I_3) = 25 - (4 + 5 + 6) = 10 \text{ A}$$

$$I_4 = 10 \text{ A}$$

$$R_4 = \frac{200}{I_4} = \frac{200}{10} = 20 \Omega$$

$$R_T = 0.125 \Omega$$

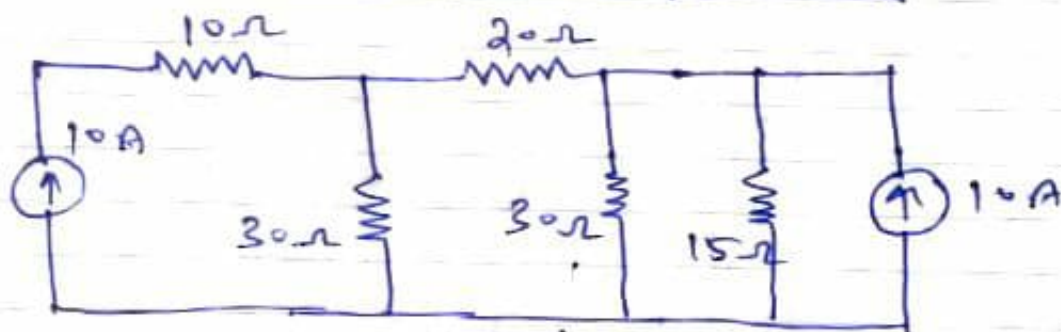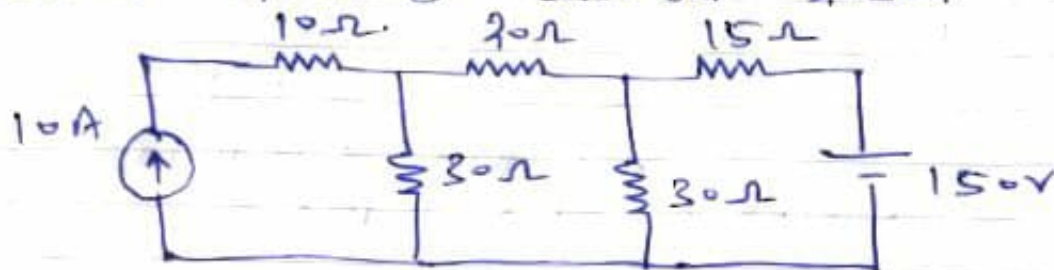
7. Evaluate the node voltages in the given circuit using nodal analysis. Also find the current flowing through 20Ω .



$$I = \frac{V}{R} = \frac{150}{15} = 10A$$

$$30\Omega \parallel 15\Omega$$
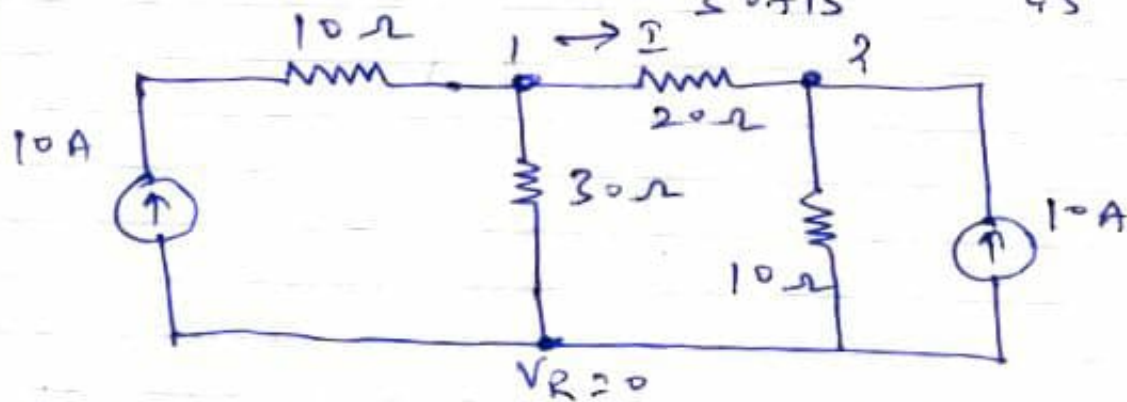
$$\frac{20 \times 15}{30 + 15} = \frac{450}{45} = 10\Omega$$



$$\begin{bmatrix} \frac{1}{10} + \frac{1}{30} + \frac{1}{20} & -\frac{1}{20} \\ -\frac{1}{20} & \frac{1}{20} + \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

$$\begin{bmatrix} 0.183 & -0.05 \\ -0.05 & 0.15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

$$\Delta = (0.183 \times 0.15) - (0.05 \times 0.05) = 0.027 - 0.0025 = 0.0245$$

$$\Delta_1 = \begin{bmatrix} 10 & -0.05 \\ 10 & 0.15 \end{bmatrix} = 10(0.15) + 10(0.05) = 1.5 + 0.5 = 2$$

$$\Delta_2 = \begin{bmatrix} 0.183 & 10 \\ -0.05 & 10 \end{bmatrix} = 0.183(10) + 10(0.05) = 1.83 + 0.5 = 2.33$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{2}{0.0245} = 81.63 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2.33}{0.0245} = 95.10 \text{ V}$$

$$I_{30\Omega} = \frac{V_1 - V_2}{20} = \frac{81.63 - 95.10}{20}$$

$$= \frac{-13.47}{20} = -0.6735 \text{ A. (Arbitrarily Direction)}$$

Node voltages

$$V_1 = 81.63 \text{ V}$$


$$V_2 = 95.10 \text{ V}$$

Current flow through the


30 Ω resistor is

$$0.6735 \text{ A.}$$

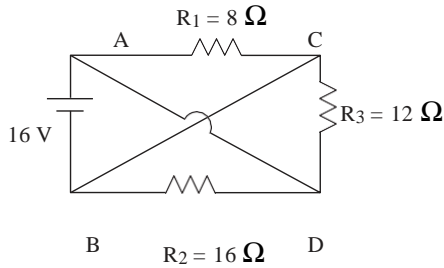8. Calculate the total resistance and battery current in the given circuit



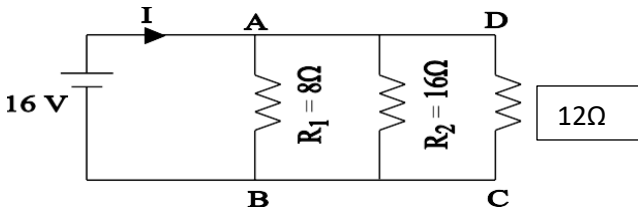The given above circuit can be re-drawn as,



$8\ \Omega$, $16\ \Omega$, $12\ \Omega$ are connected in parallel. Its equivalent resistance,

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

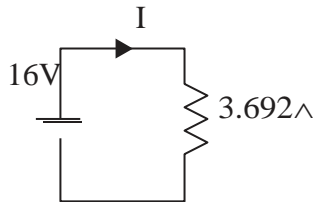



Figure 1.28

$$R_T = \frac{8 \times 16 \times 12}{128 + 192 + 96} = 3.692\ \Omega$$


$$R_T = 3.692\ \Omega$$

$$I = \frac{V}{R} = \frac{16}{3.692} = 4.33\text{A}$$

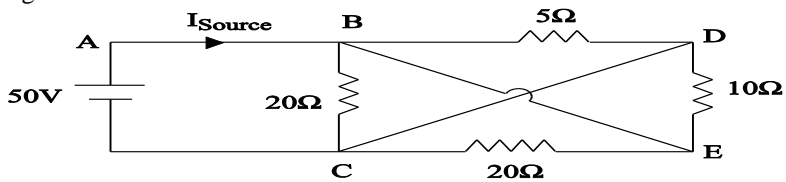9. Calculate the equivalent resistance offered by the circuit to the voltage source and also find its source current



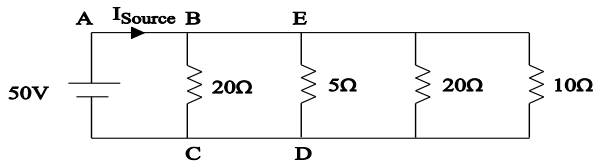
Solution: The given above circuit can be re-drawn as



$20\ \Omega$ and $10\ \Omega$ resistors are connected in parallel, its equivalent resistance is


given by, $\frac{20 * 10}{20 + 10} = 6.667\ \Omega$

The given circuit is reduced as,

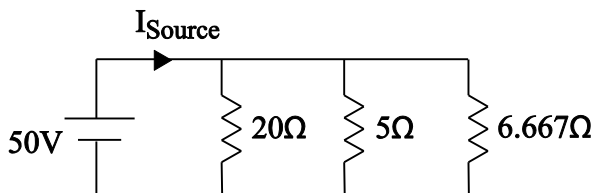

6.667 Ω and 5 Ω resistors are connected in parallel, its equivalent resistance is given by, $\frac{6.667 * 5}{6.667 + 5} = 2.857 \Omega$


The circuit is reduced as,

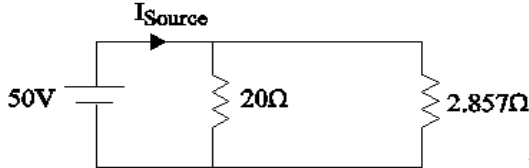

20 Ω and 2.857 Ω are connected in parallel. Its equivalent resistance is,

$$\frac{20 * 2.857}{20 + 2.857} = 2.497 \Omega$$

The Circuit is re-drawn as,

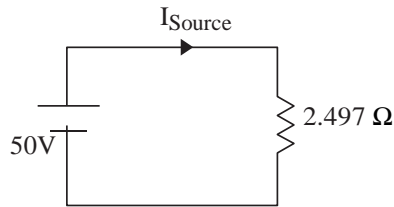


Hence the equivalent resistance of the Circuit is $R_T = 2.497 \Omega = 2.5 \Omega$

Source Current of the Circuit is given by,


$$I_{source} = \frac{V}{R} = \frac{50}{2.5} = 20A$$

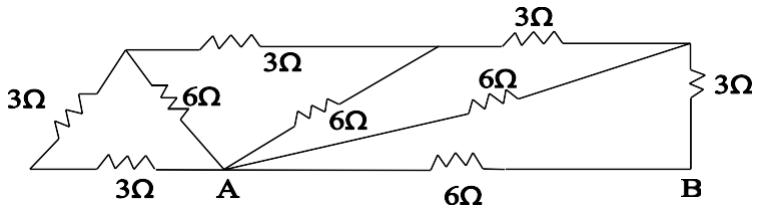10. Find the equivalent resistance between the terminals A and B.




Solution:

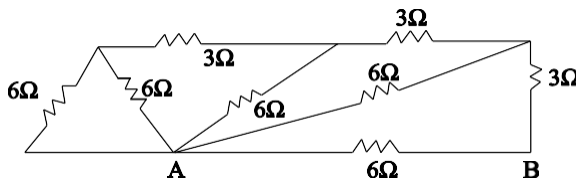3 Ω and 3 Ω are connected in Series, it equivalent resistance is, $(3 + 3) = 6 \Omega$.
The Circuit gets reduced as




6 Ω and 6 Ω are connected in parallel. The circuit gets reduced as,
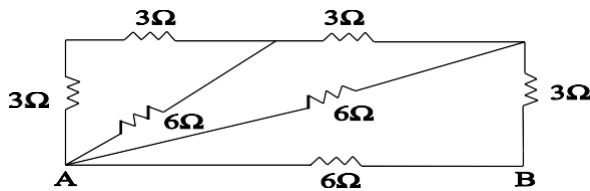
$$\frac{6 \times 6}{6 + 6} = 3 \text{ ohms.}$$




3 Ω and 3 Ω are connected in series $(3 + 3 = 6 \Omega)$.

The reduced Circuit is,

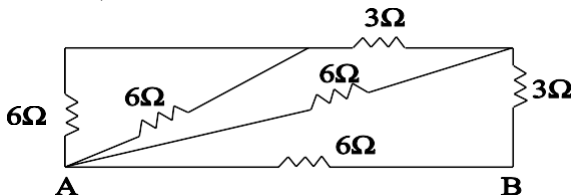


$6\ \Omega$ and $6\ \Omega$ are connected in parallel. Its equivalent resistance, $\frac{6*6}{6+6} = 3\ \Omega$



The circuit can be reduced as,

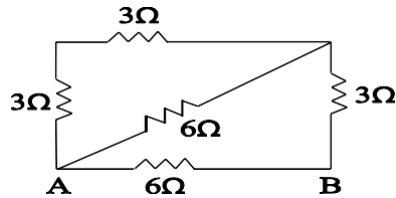

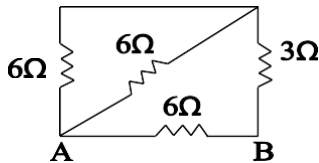$3\ \Omega$ and $3\ \Omega$ are connected in series. ($3 + 3 = 6\ \Omega$).



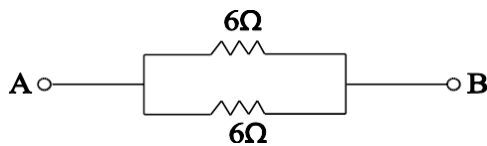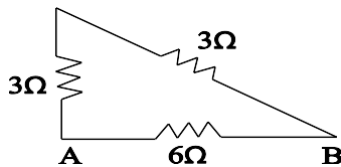$6\ \Omega$ and $6\ \Omega$ are connected in parallel. Its equivalent resistance, $\frac{6*6}{6+6} = 3\ \Omega$



$3\ \Omega$ and $3\ \Omega$ are connected in series, the reduced Circuit is $3 + 3 = 6\ \Omega$

$6\ \Omega$ and $6\ \Omega$ are connected in parallel.

The equivalent resistance between the terminals A and B

given by $R_{AB} = 3\ \Omega$.

$3\ \Omega$



$$\therefore R_{AB} = 3\ \Omega$$